
PiedPiperS circuit

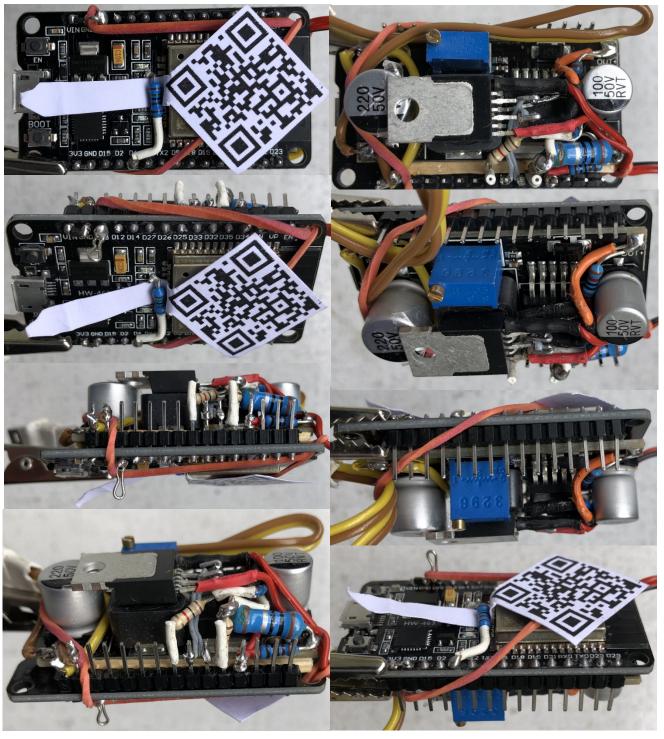
ESP32 DevKit V1, step-up converter and TLE5206-2S motor driver, incl. power measuring resistors




https://github.com/jorail/PiedPiperS, v175, 2021-05-01, GNU GPL v3, © J. Ruppert

ESP32 & TLE5206-2S

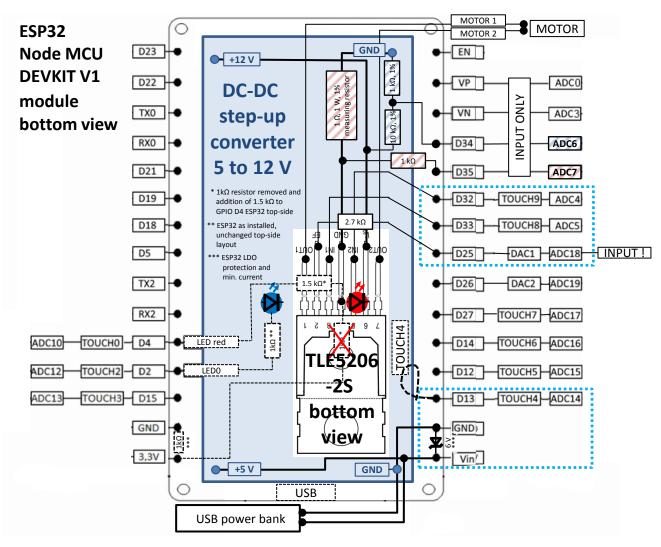integrated mounting and wiring with LDO protection, incl. optional measuring resistors for power data reading



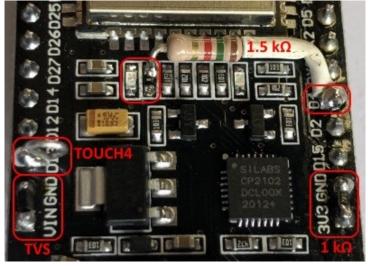

ESP32 Node MCU DEVKIT V1 module top view:

- power LED modification by 1.5 kΩ resistor to D4 pin
- TOUCH4 pin wire loop
- TVS diode 6 V and load by 1 kΩ resistor at 3.3 V for LDO protection

PiedPiperS, version 173, <u>GNU GPL v3</u>, J. Ruppert 2021-04-28, <u>https://github.com/jorail/PiedPiperS</u>