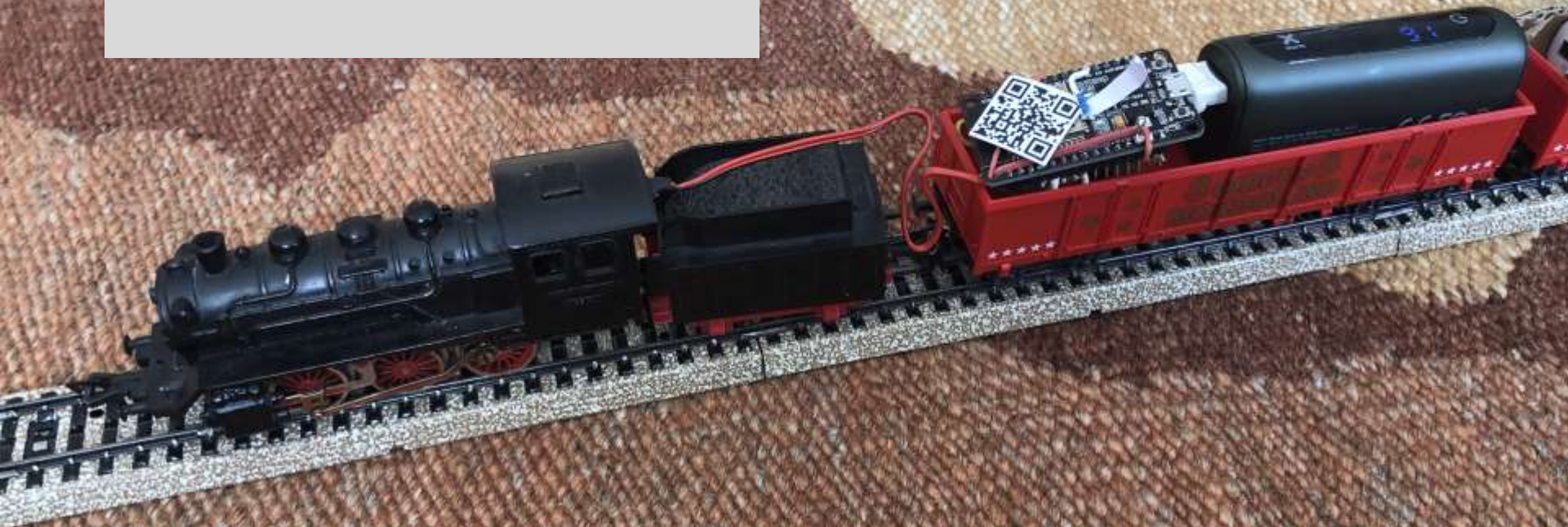


# PiedPiperS


smartphone speed control  
for model trains



- Outdoor compatible, on-board USB power supply independent of track current
- ESP32 microprocessor, C++ Arduino software, with WIFI Access Point and Webserver
- No proprietary elements, construction time 1 weekend, material cost ca. 25 €

# Train control website on smartphone



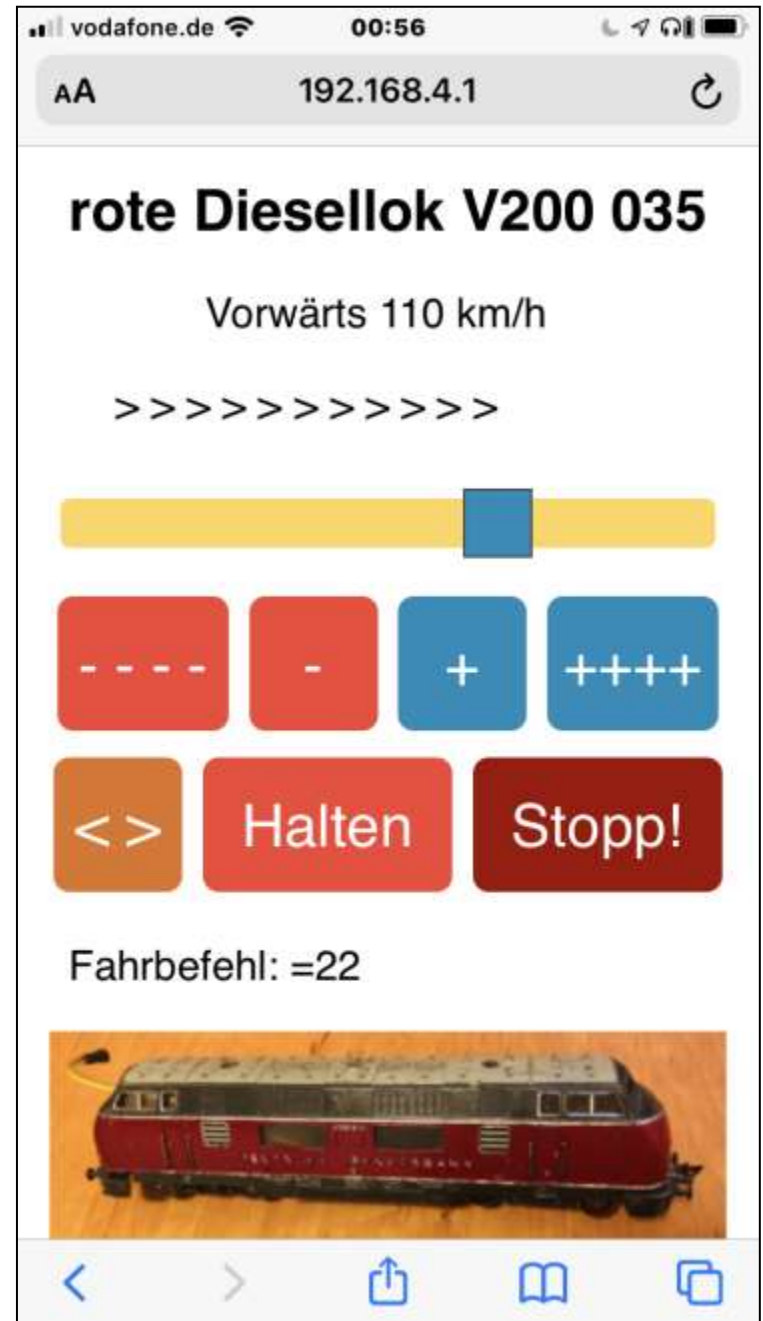







- Compatible with every smartphone with WIFI
- ESP32 WIFI access point mounted on train
- Browser access to control panel via Webserver
- Stable remote controle for up to two users
- Additional manual control via touch pin
- Feedback from train operation on two LEDs
- Motor IC error handling, short cut protection
- ESP32 voltage spike and brownout protection
- Option for online power measurement and data display in tables and charts
- Option for true speed measurement by IR sensor detection of railway sleepers



# PiedPiperS touch commands

Touch code	Command for speed level	Meaning
•	--	decrease speed
••	-----	slow down
•••	-----	break to halt
••••	0	fast brake and stop
•••••	00<	fast stop, reverse direction
• —	++	increase speed
• — —	+++++	speed up
• — — —	+++++	go fast
—	0	fast brake and stop
— —	00	fast brake and stop
————	00	fast brake and stop
— — —	?	info?


# PiedPiper LED indicators

	LEDs  
Information on motor direction and speedlevel: <ul style="list-style-type: none"> <li>• forward = 1 = green LED + 0 to 16 short LED flashes</li> <li>• backward = 0 = red LED + 0 to 16 short LED flashes</li> </ul>	 
Adjustment of motor speed: <ul style="list-style-type: none"> <li>• 2 green LED flash = speed level + 2;</li> <li>• 2 red LED flash = speed level - 2;</li> <li>• green &amp; red LEDs long flash = fast brake, speed level = 0</li> </ul>	  
Change of motor direction: <ul style="list-style-type: none"> <li>• green/red/green + green LED flash = forward = 1</li> <li>• red/green/red + red LED flash = backward = 0</li> </ul>	 
Program running and main loop frequency: <ul style="list-style-type: none"> <li>• orange flash after 5,000 main loop cycles, 200 times monitoring for input activity and up to 5 speed adjustments</li> </ul>	



# PiedPiperS project development

<https://github.com/jorail/PiedPiperS>

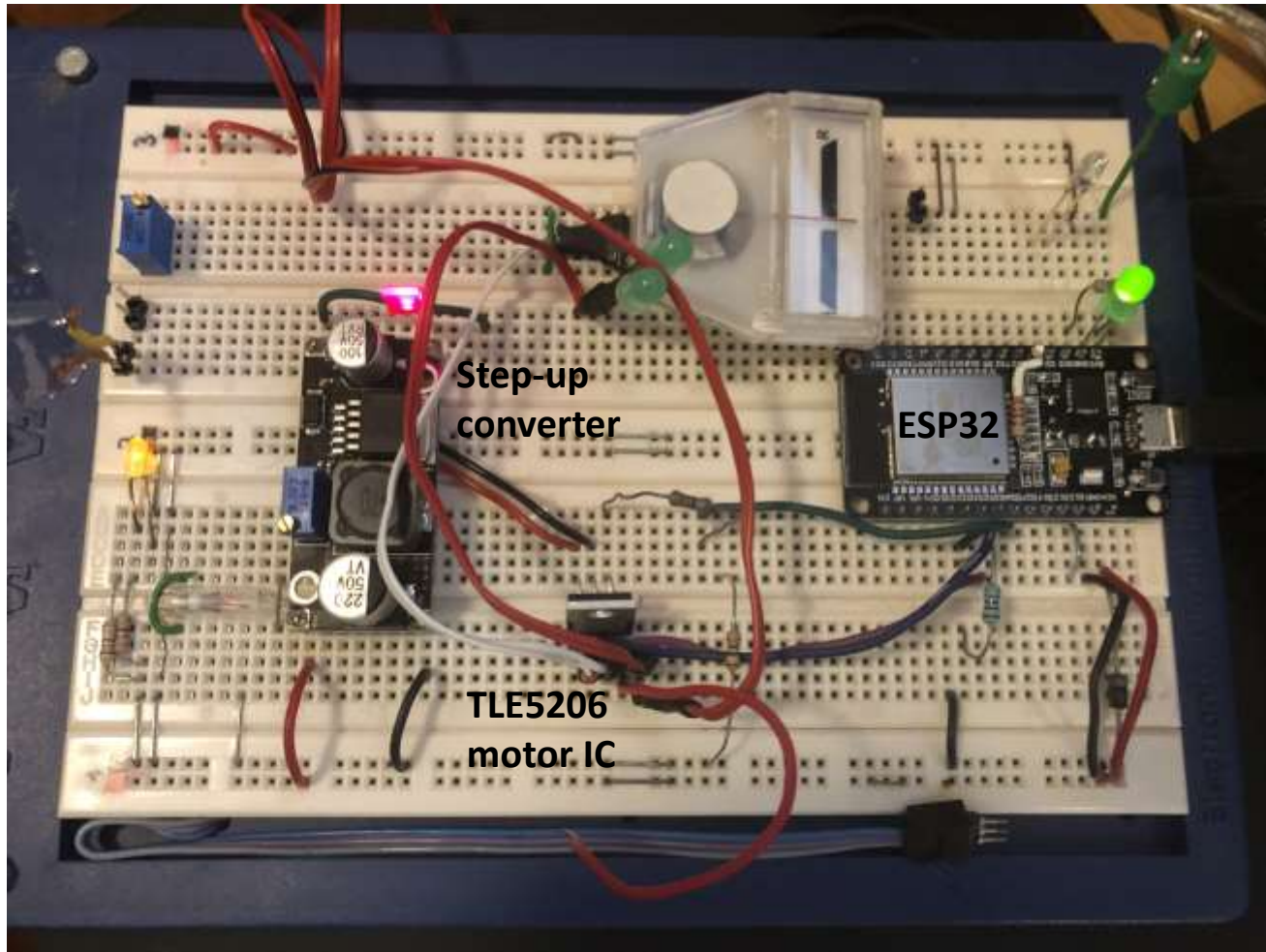

# Material demand

## for 1 train with WiFi control

### Electronics

- Nano size microcontroller with WiFi  
e.g. ESP32 DevKit V1, etc.
  - 2 PWM outputs for motor control
  - 2 digital outputs for LED indicators
  - 1 digital input for touch switch
  - 1 digital input for motor IC error flag
- Step-up DC/DC converter module, 5 V to 12V ... 16 V
- H-Bridge DC motor control IC, e.g. TLE5206-2S
- Small size USB power bank as 5 V DC power supply  
it is good to have two, 2<sup>nd</sup> for replacement when 1<sup>st</sup> empty
- Shrink tube with diameter for holding two IC pin contacts
- Thick USB cable, old and used, but reliable for power connection with small voltage drop
- Reuse of 2 on-board LEDs, by soldering 1.5 K $\Omega$  resistor from pin  
(or alternatively LEDs: 1 blue, 1 red, 3 mm diameter plus 2 x 1.5 K $\Omega$  resistors)
- 2.7 k $\Omega$  resistor, protection for digital input
- 1 k $\Omega$  SMD resistor as artificial load after LDO
- 1 SMD TVS-diode, 5 V reverse working (standoff) voltage as protection of 5 V input from peak voltages of the Step-up converter
- 2 pole cable, thin and flexible, ca. 40 cm, for connection to motor
- 1 pole wires for breadboard and step up converter connections, ca. 20 cm in total

### Other material

- Model train locomotive with 12V ... 16 V DC motor
- Flat wagon for electronics equipment
- Eaos high board open wagon for USB power bank
- Some paper cardboard
- Single and double sided adhesive tape

### Tools

- Very fine tip solder iron with equipment
- Cutter, fine pincers
- Multi-meter tool

### Option 1 addition


- ESP32 DevKit V1
  - 2 analog inputs for voltage and current readings
- Measuring resistors 1  $\Omega$ , 1 k $\Omega$ , 10 k $\Omega$ , tolerance 1%
- 1 k $\Omega$  resistor, protection for analog input

### Option 2 addition

- ESP32 DevKit V1
  - 1 analog input for amplified IR sensor voltage reading
- Suitable reflective IR sensor
- IR LED resistor
- Signal amplifier with small transistor and pullup resistor

Estimated material cost ca. 25 € excl. other material, tools and optional additions


# Main electronic parts

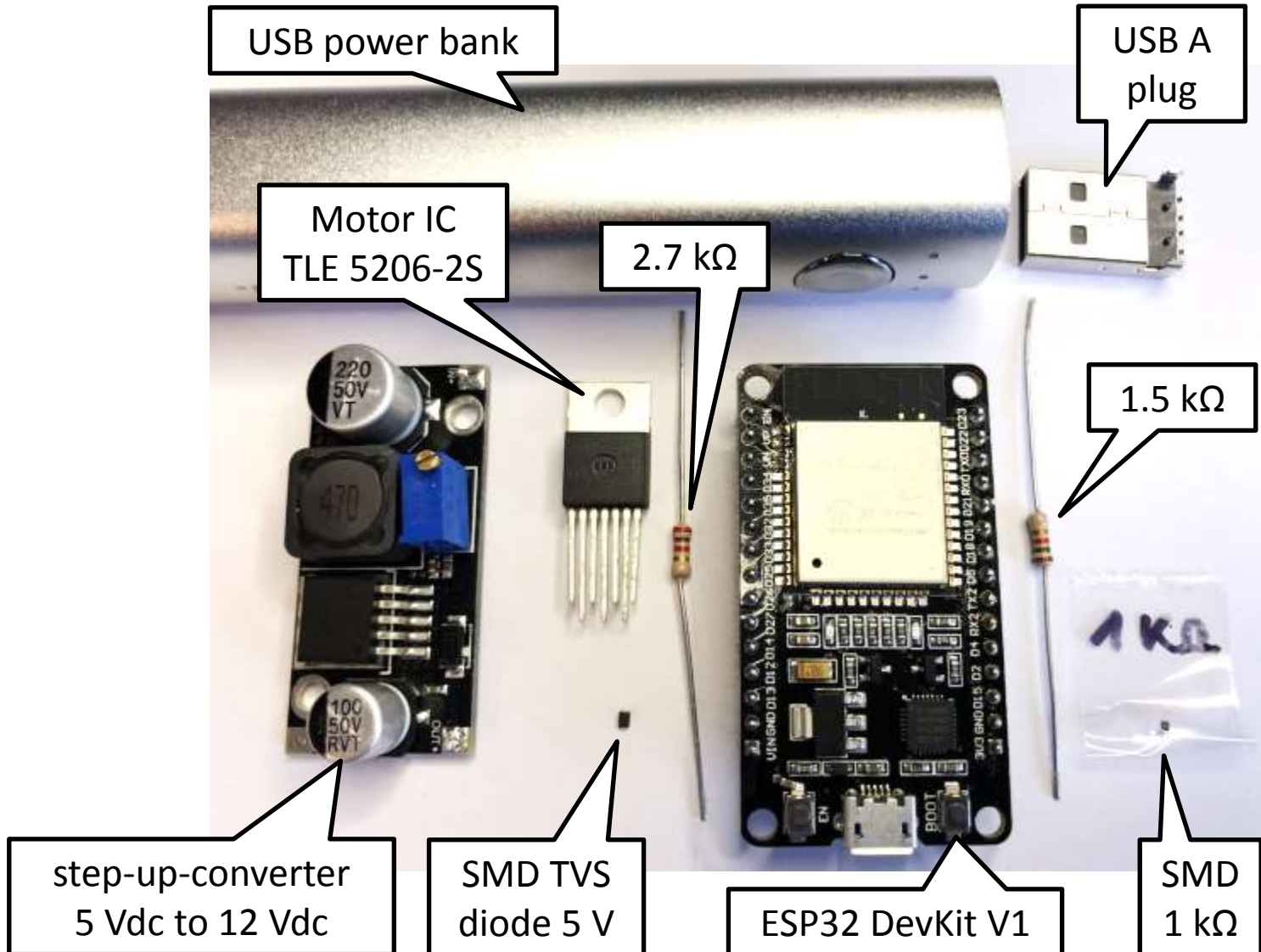
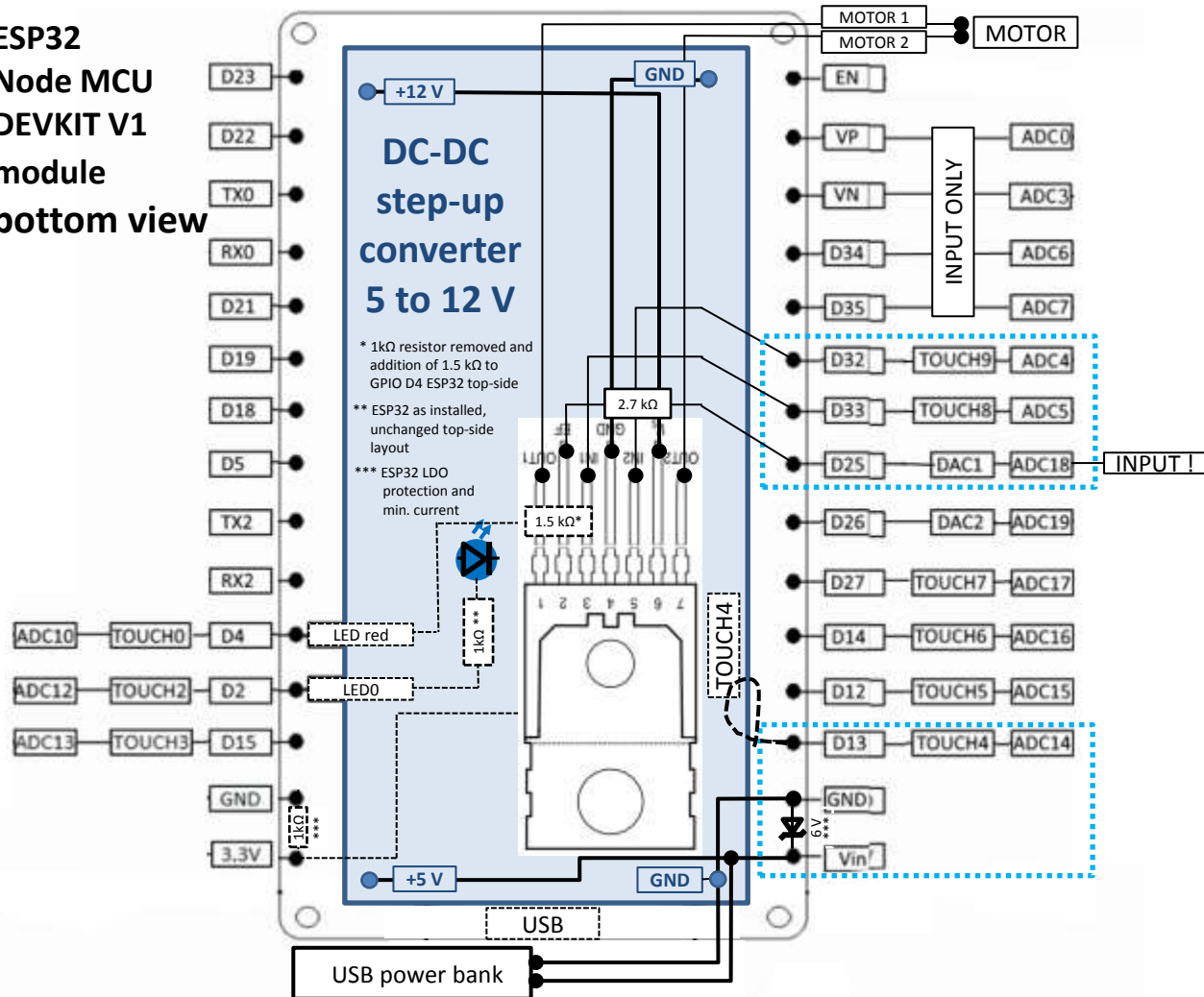
# ESP32 & TLE5206-2S

integrated mounting and wiring with LDO protection, v100

ESP32  
Node MCU  
DEVKIT V1  
module  
bottom view







# Required tools



# Material for ESP32 topside adjustment



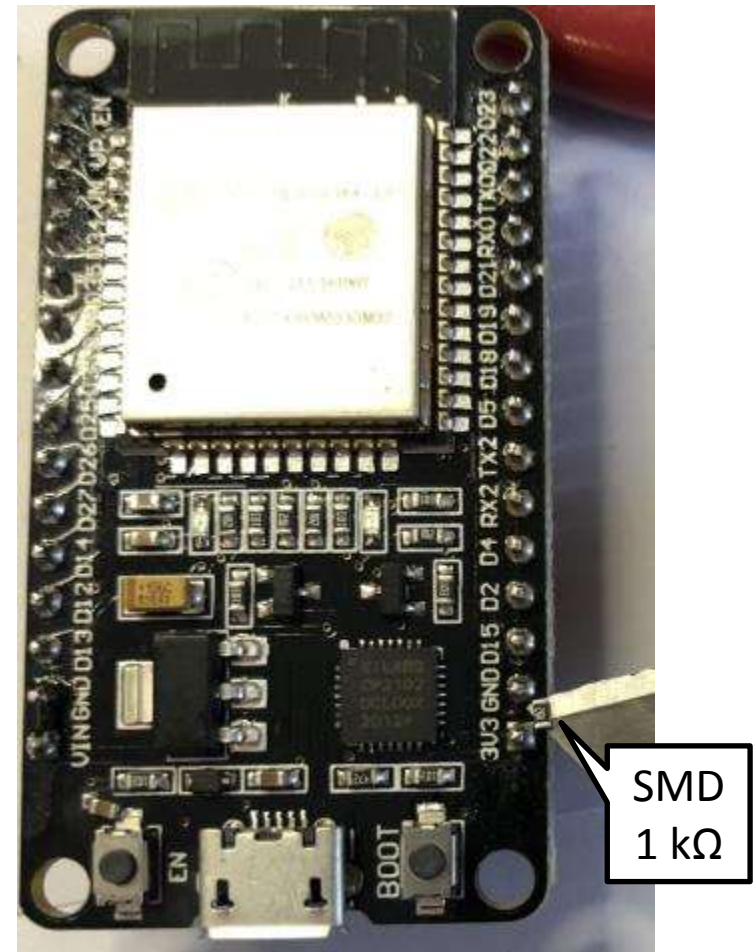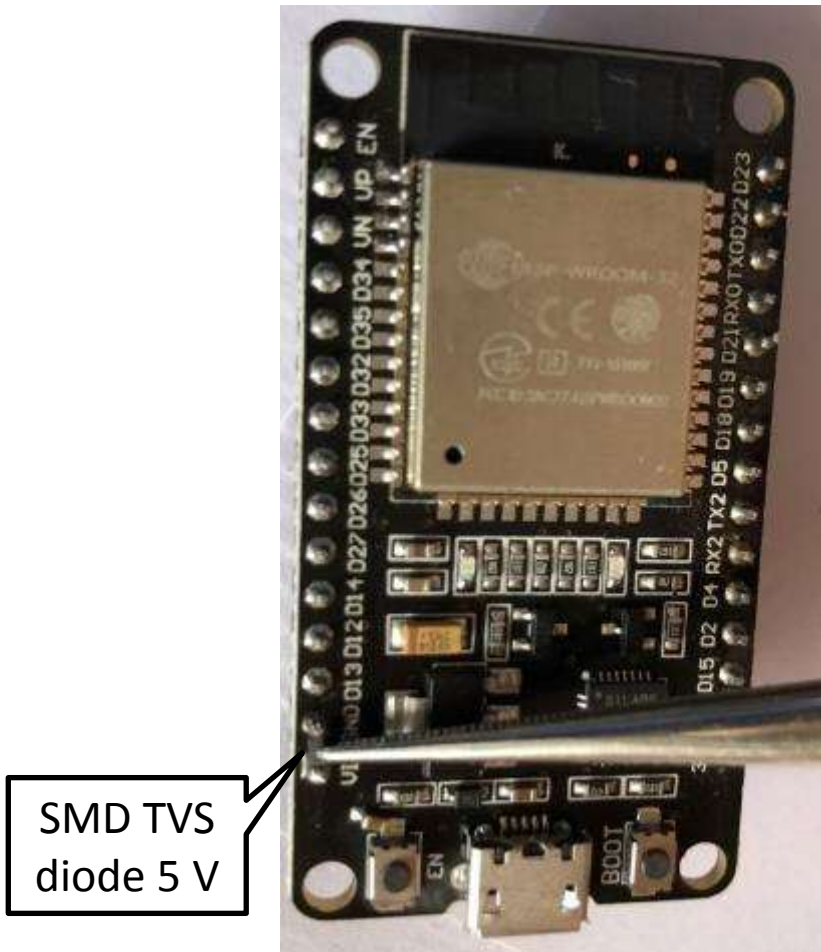
# Solder SMD elements at 5 V input and 3.3 V output





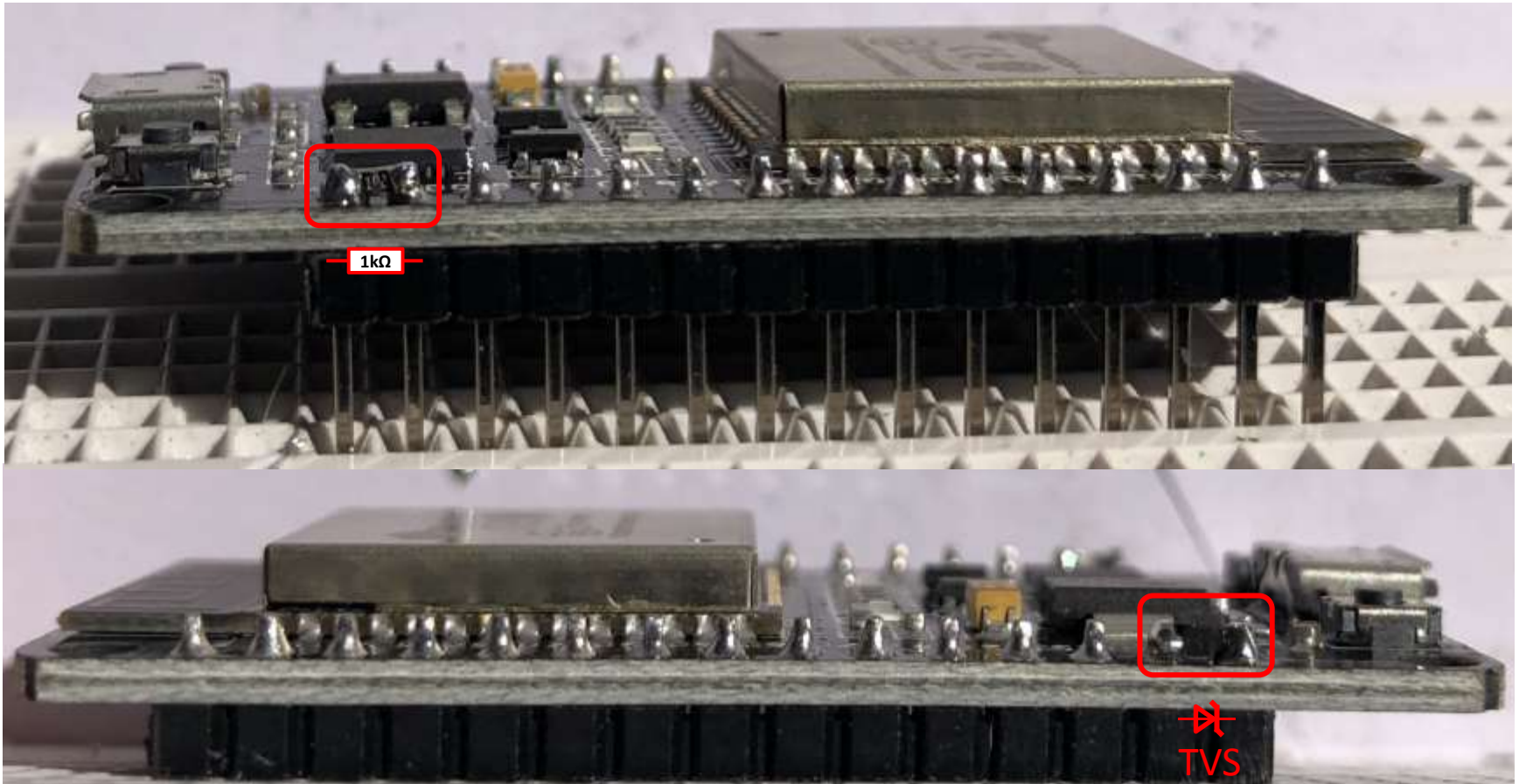
# SMD resistor and TVS diode at power pins




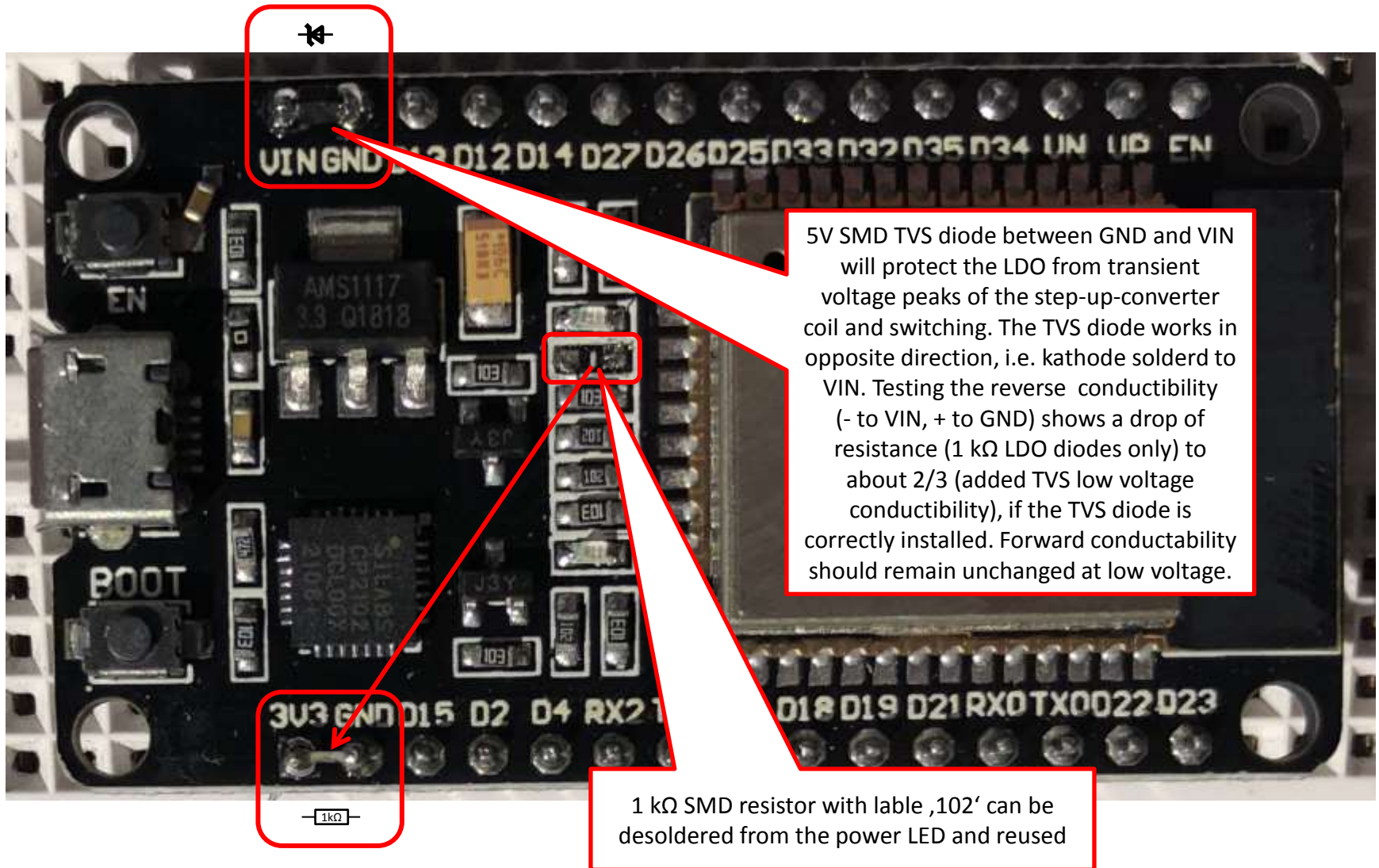
# Protecting ESP32 for power supply from USB power bank linked to step-up-converter



5V SMD TVS diode between GND and VIN will protect the LDO from transient voltage peaks of the step-up-converter coil and switching. The TVS diode works in opposite direction, i.e. cathode soldered to VIN. Testing the reverse conductivity (- to VIN, + to GND) shows a drop of resistance (1 kΩ LDO diodes only) to about 2/3 (added TVS low voltage conductivity), if the TVS diode is correctly installed. Forward conductivity should remain unchanged at low voltage.



1 kΩ SMD resistor with lable ,102' can be desoldered from the power LED and reused

# Soldering 1 k $\Omega$ resistor assuring LDO load and protection



1 k $\Omega$  SMD resistor between 3.3V and GND assures a minimum current and load behind the low-dropout regulator (LDO) and its ability to regulate and protect the 3.3 V level from input voltage peaks in case of brownout. The initial total resistance of 2 k $\Omega$  between the 3.3 V and GND pins will drop to about 650  $\Omega$  after successful installation of the 1 k $\Omega$  resistor.

1k $\Omega$

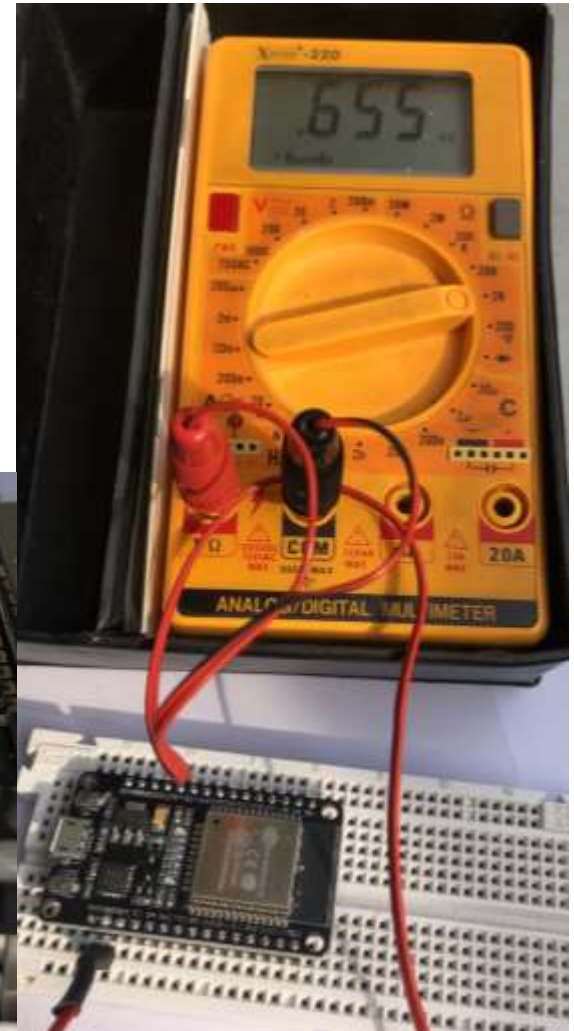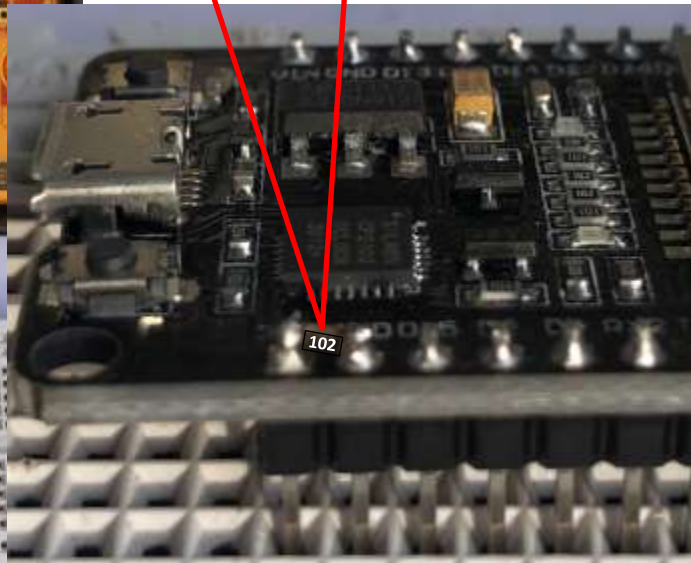




# Connecting red LED to GPIO pin D4



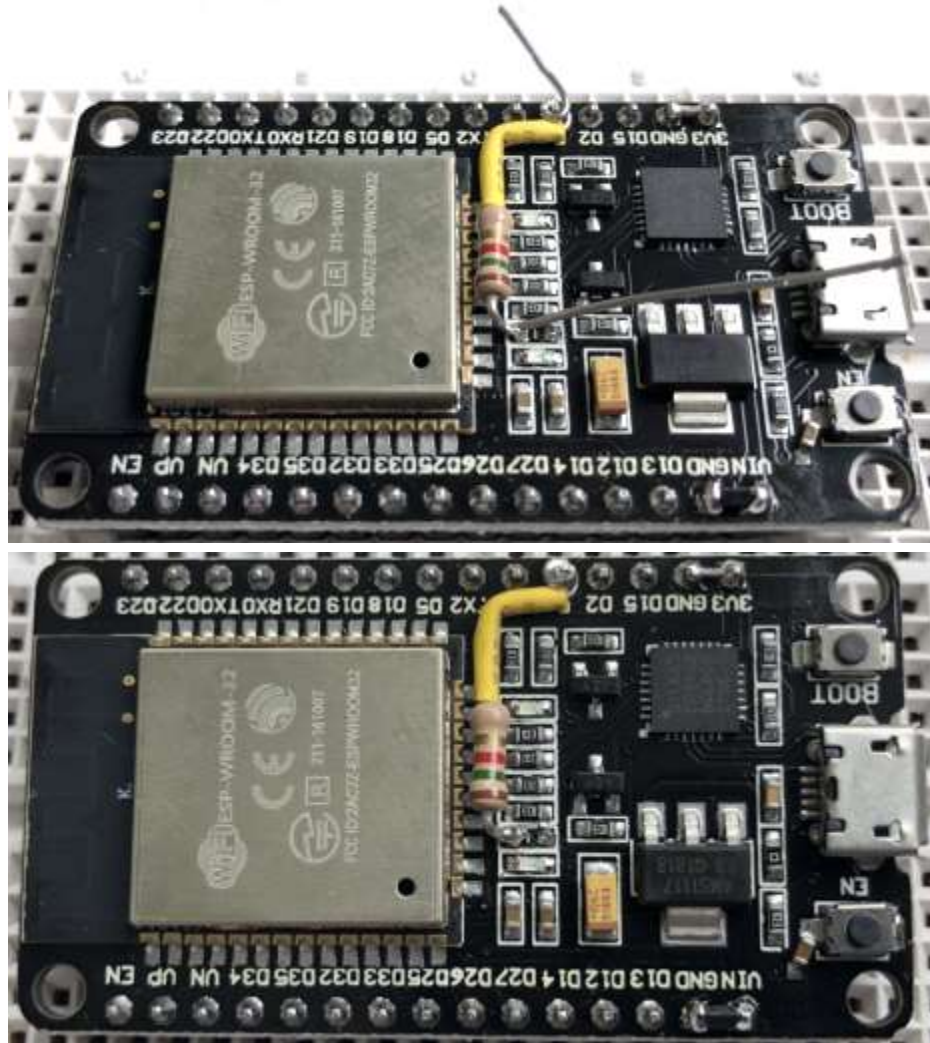1.5 kΩ resistor connects GPIO pin D4 to the de-solderd pad connecting to the red power LED. Use some small shrink tube to protect the wire from unintended contacts. Do not cover the blue LED corresponding to D2.




# Installing a manual Touch input



Solder a very small loop of strong wire to GPIO pin D13 as TOUCH4 input for manual commands to the model train (instead of a manual switch)




# ESP32 DEVKIT V1 top view

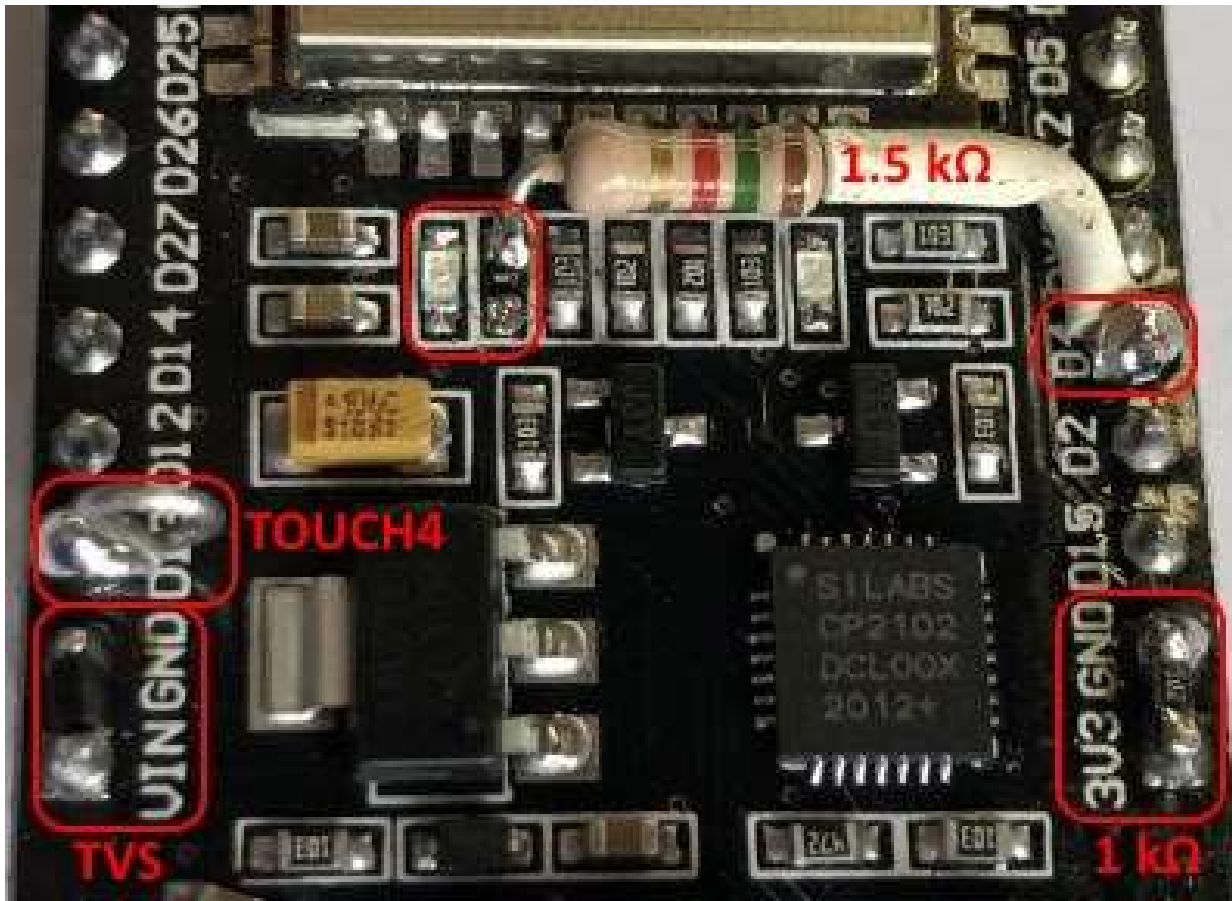



- power LED modification by 1.5 kΩ resistor to D4 pin
- TOUCH4 pin wire loop
- TVS diode 5 V and load by 1 kΩ resistor at 3.3 V for LDO protection


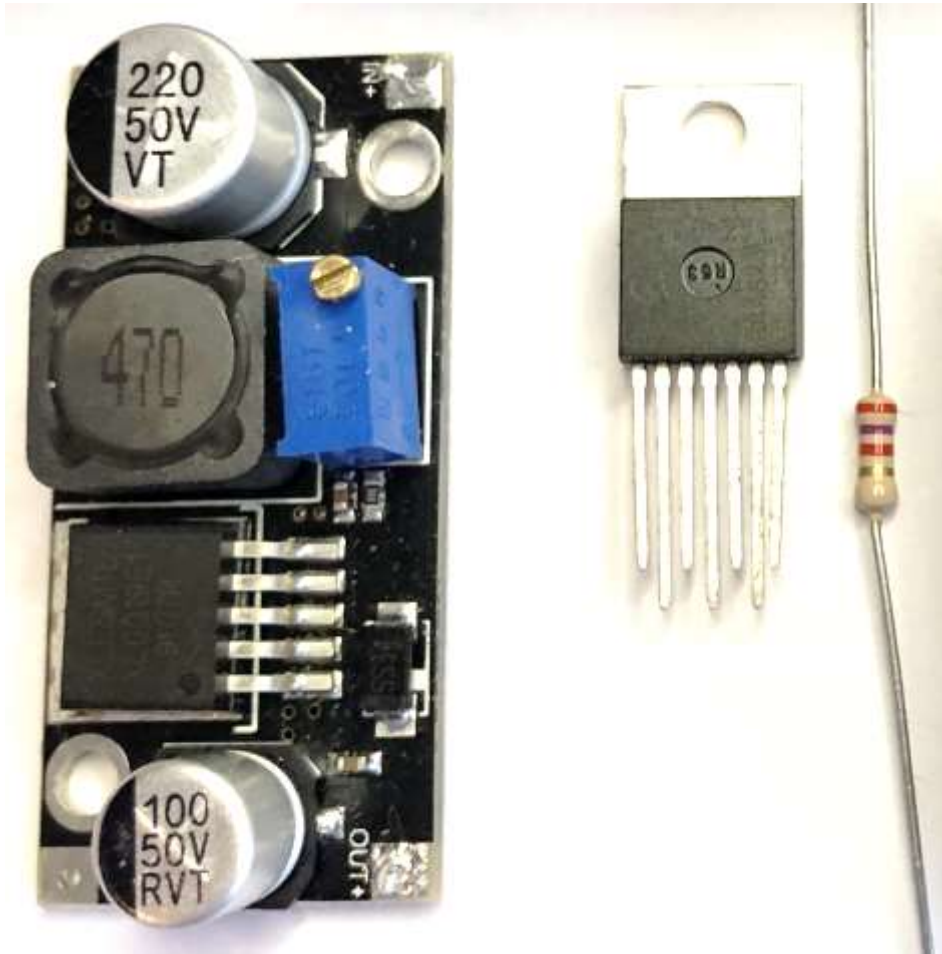
# Materials for motor control

step-up-converter and motor IC fitting at ESP32 bottom



# Mounting motor power control IC

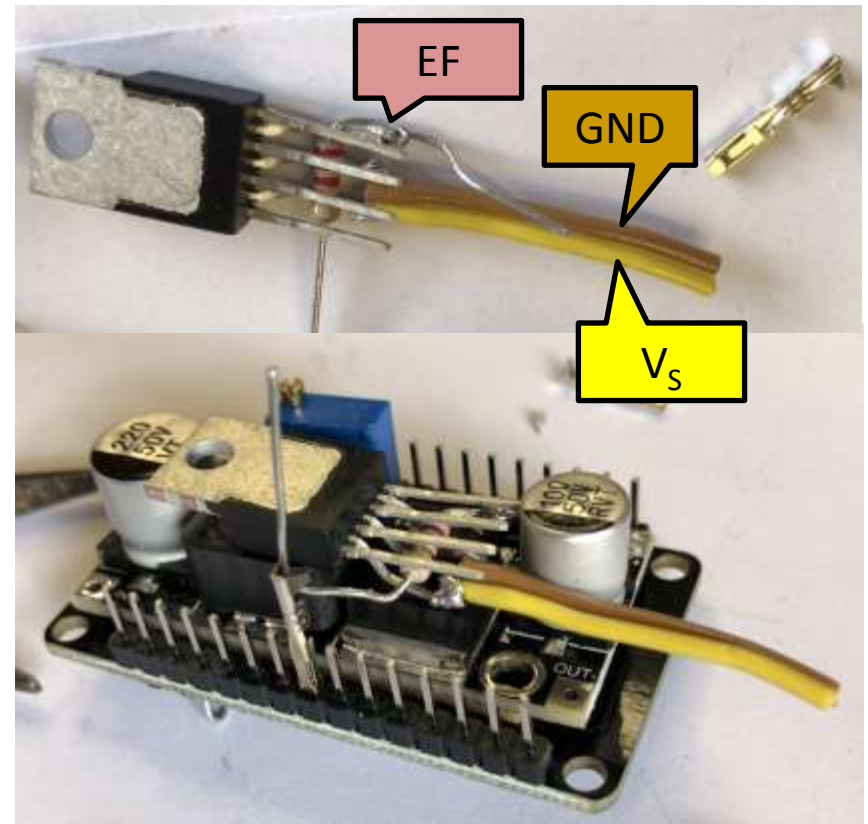
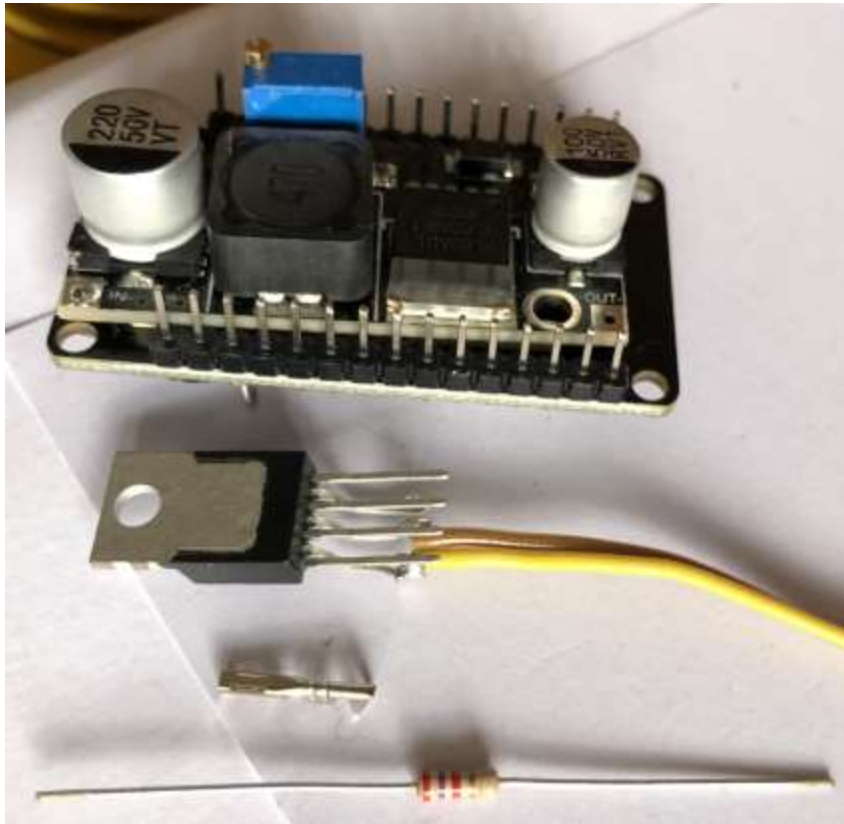


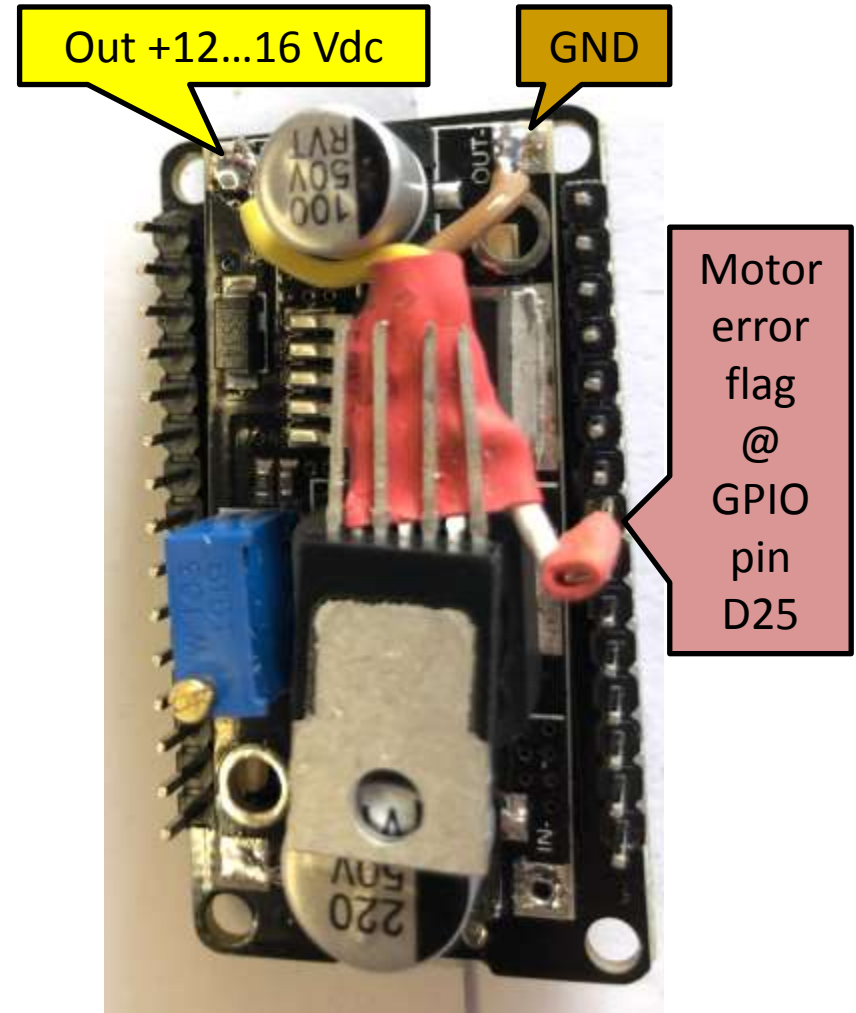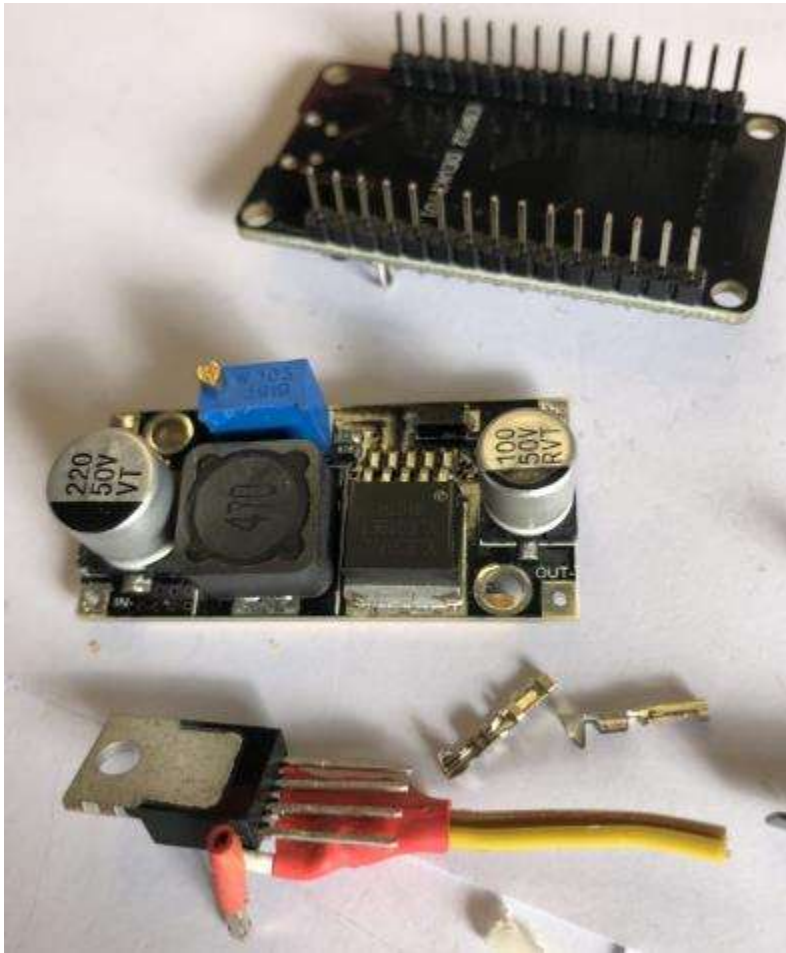



Motor  
error  
flag  
@  
GPIO  
pin  
D25



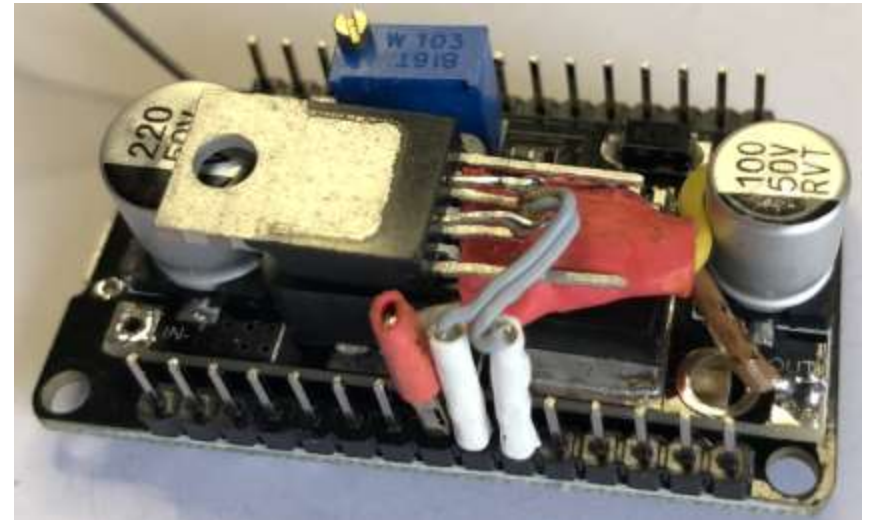
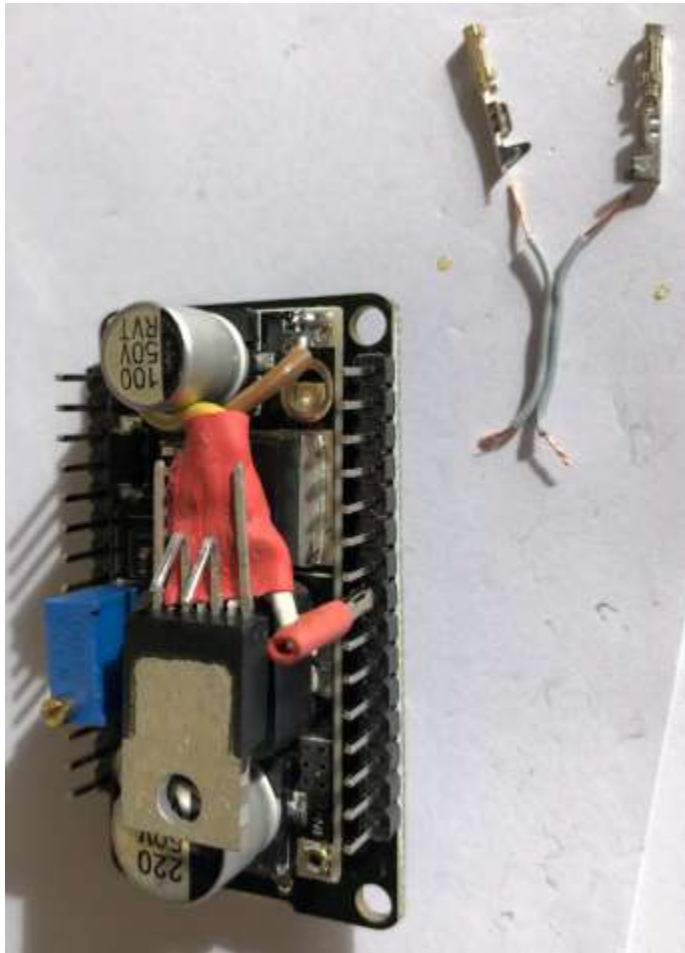
# Connect ESP32 GPIO pins D33 and D32 to motor IC IN1 and IN2


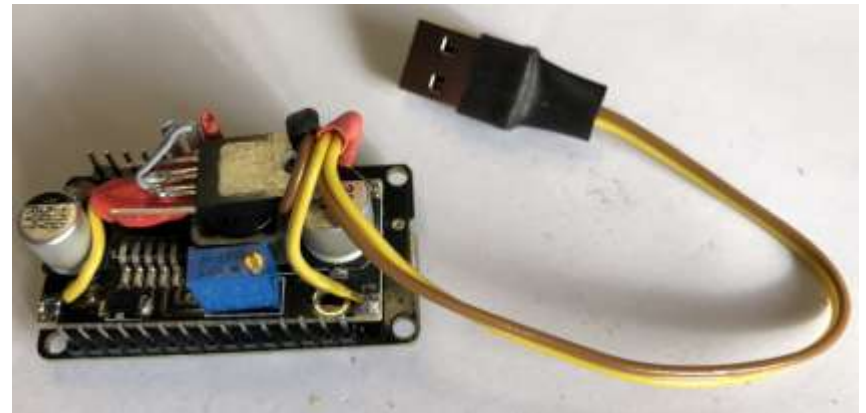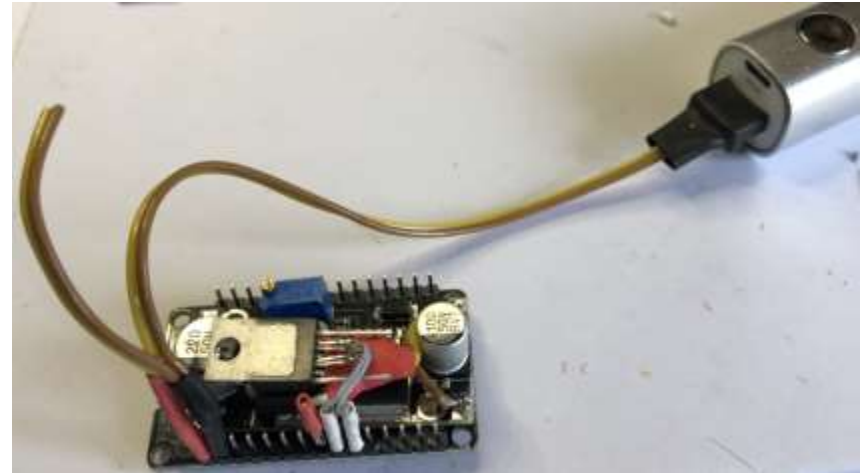
# Connect USB power bank to ESP32 VDD, GND and In+, In- of Step-up-converter


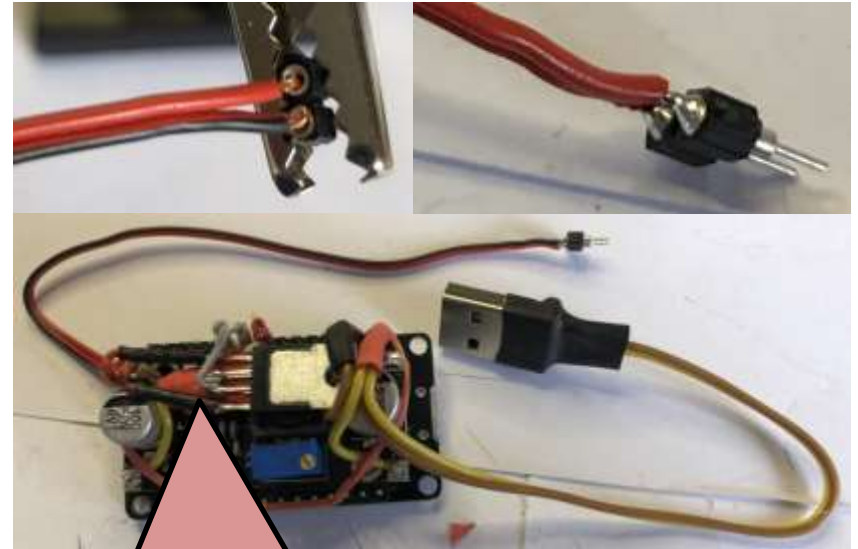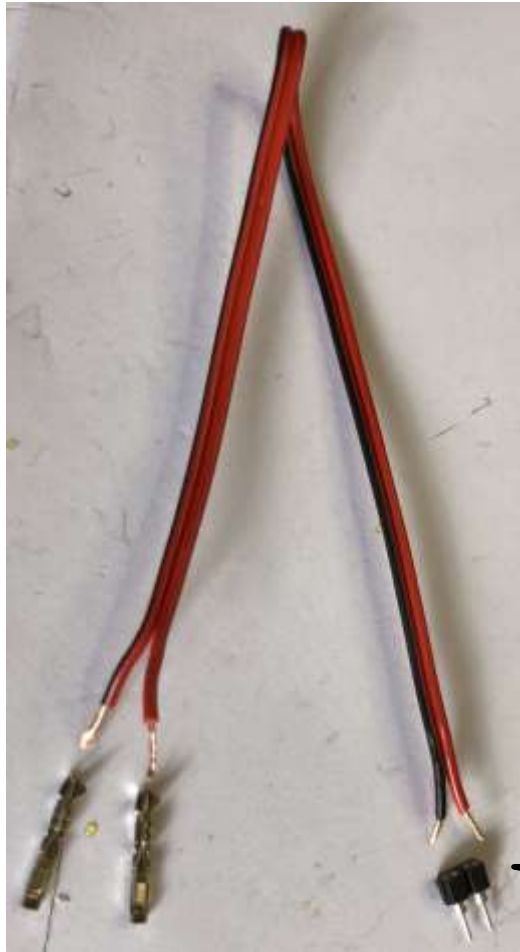
# Cable with self-made mini plug for connection to locomotive motor




Insulate and connect motor cable to motor IC OUT1 and OUT2

Self made male mini plug for connection to locomotive motor



# Completing ESP32 motor control module

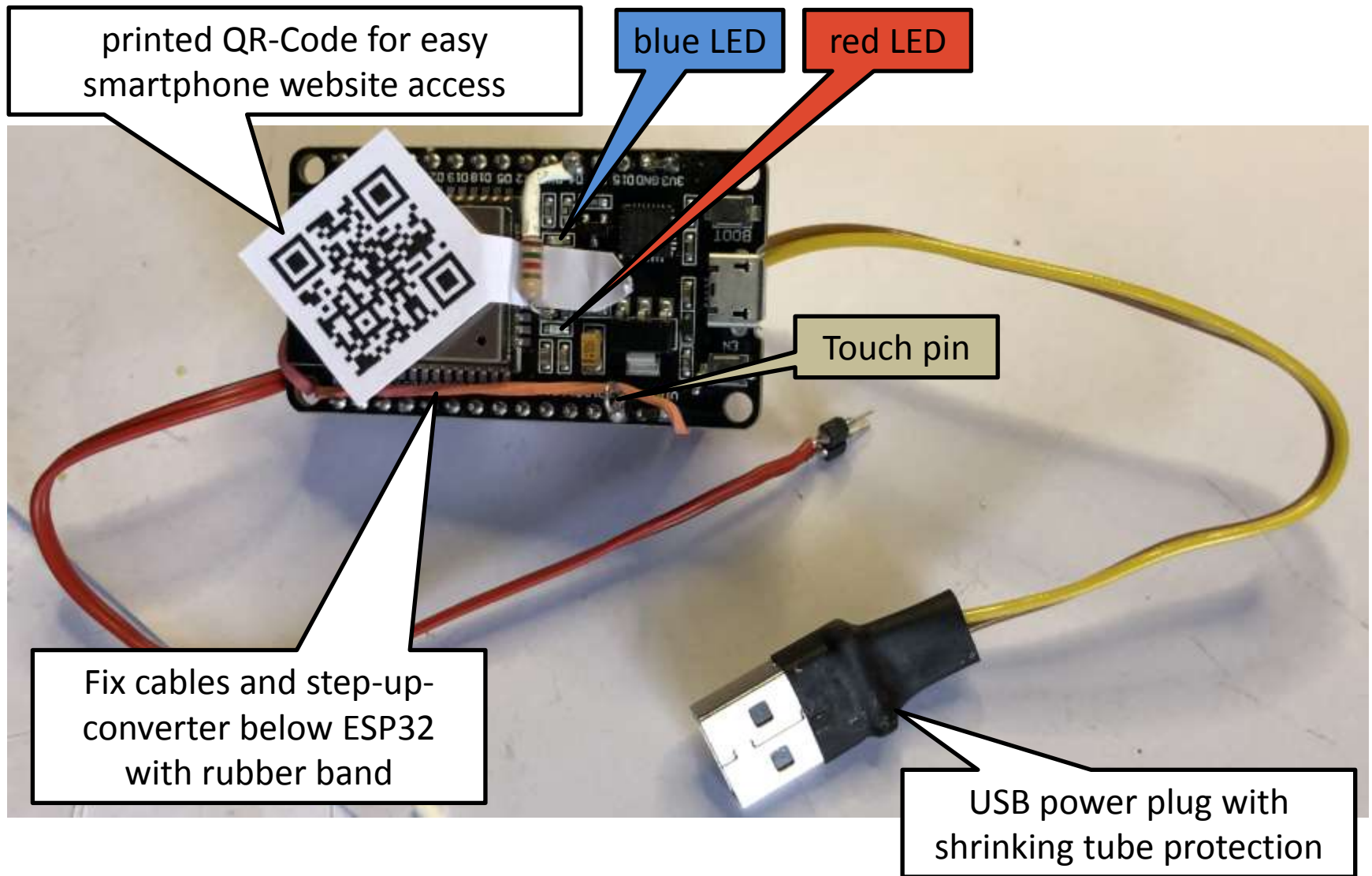




# Upload the PiedPiperS sketch and test the motor control


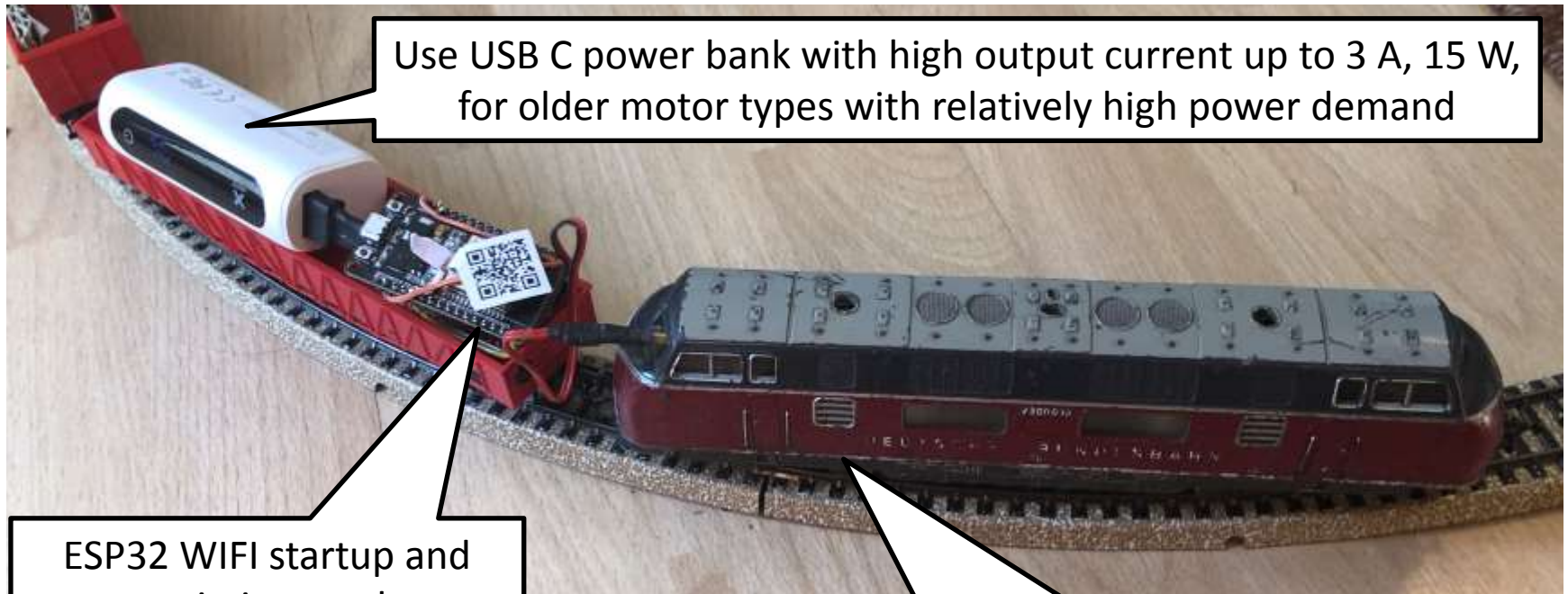
# Complete mounting on first wagon behind locomotive



Use USB C power bank with high output current up to 3 A, 15 W, for older motor types with relatively high power demand

ESP32 WIFI startup and transmission can have significant power demand, reported up to 500 mA

Train can run completely independent of rail power supply.

If more than one train is running, cut internal connection to rail power.

# Option 1: Power sampling


by reading current and voltage on measuring resistors


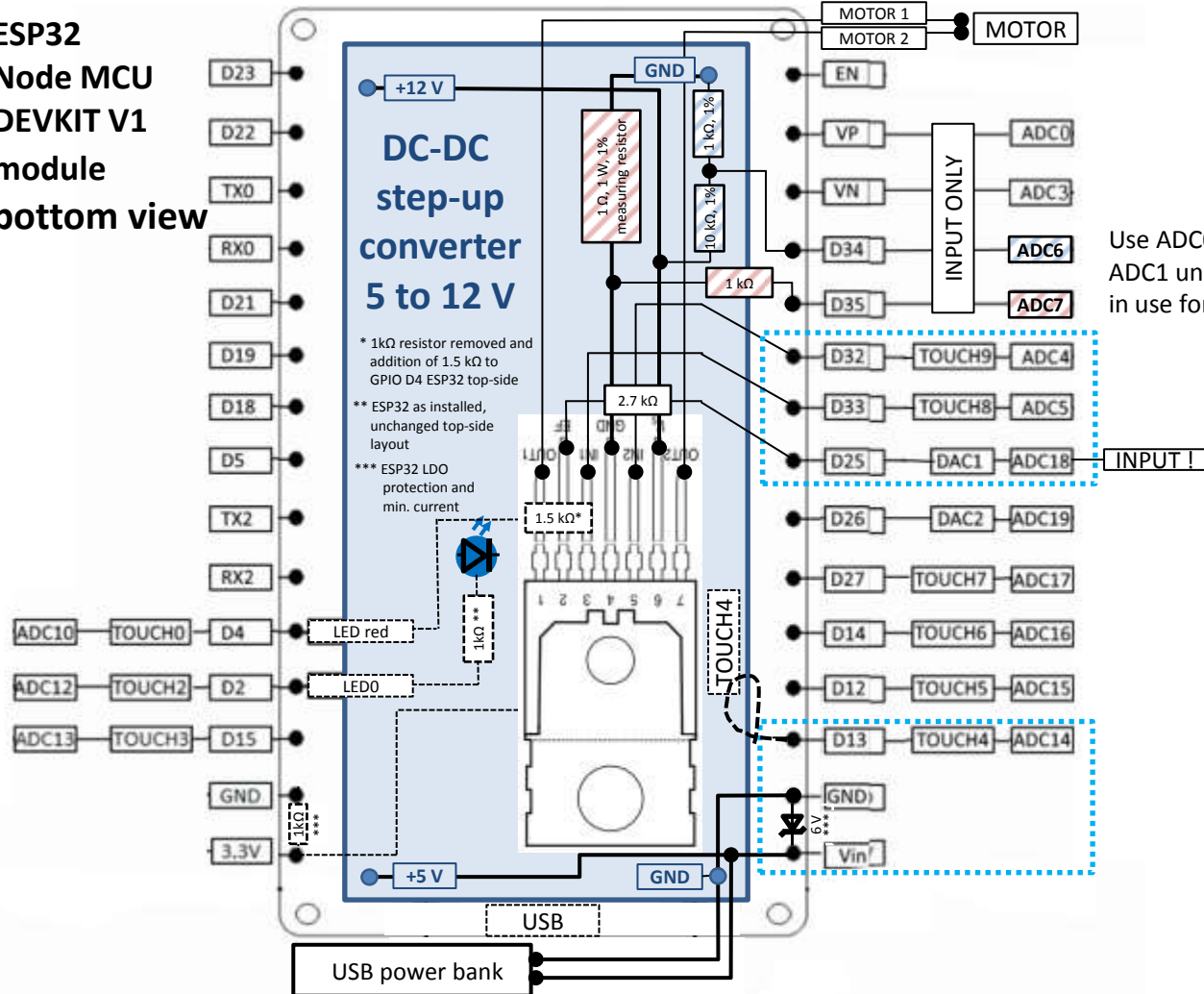
# ESP32 & TLE5206-2S

integrated mounting and wiring with LDO protection,  
v173 including optional measuring resistors for power data reading



ESP32  
Node MCU  
DEVKIT V1  
module  
bottom view



Use ADC0 unit channels only  
ADC1 unit channels are already  
in use for wifi operation!



INPUT !

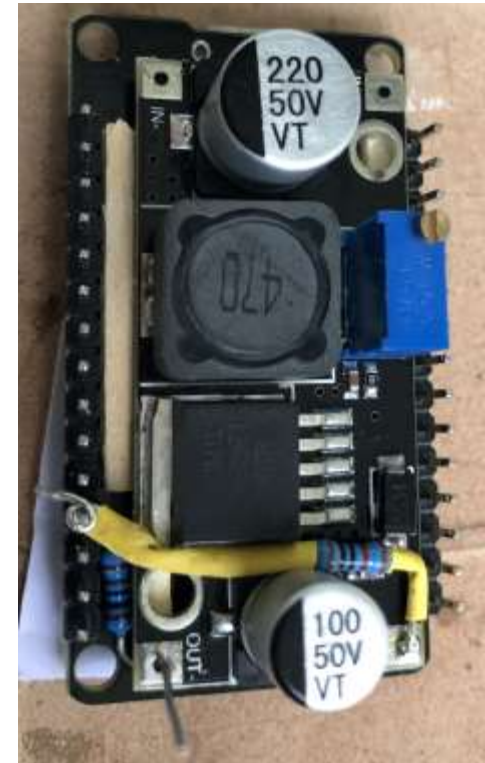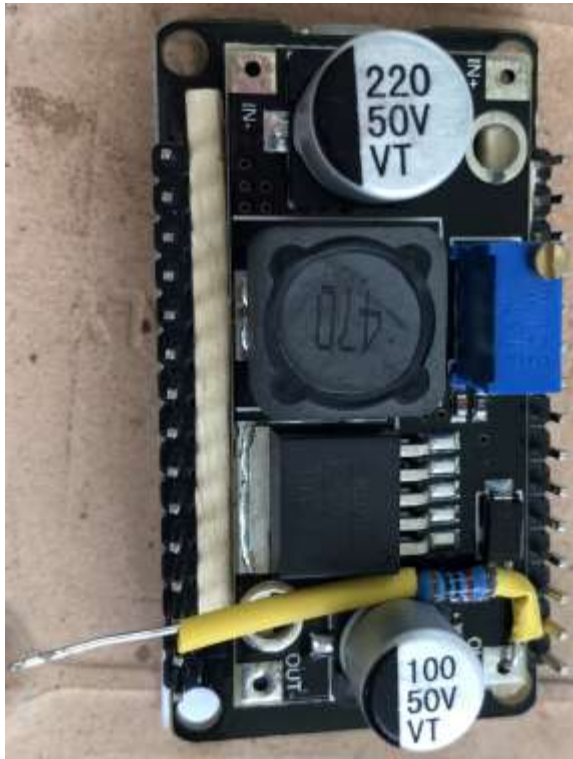Voltage measurement from divider between OUT+ and OUT- of step-up-converter consisting of 10.0 k $\Omega$  and 1.00 k $\Omega$  measuring resistors (1% tolerance), connected to GPIO pin D34




Isolation with 1 mm shrinking tube
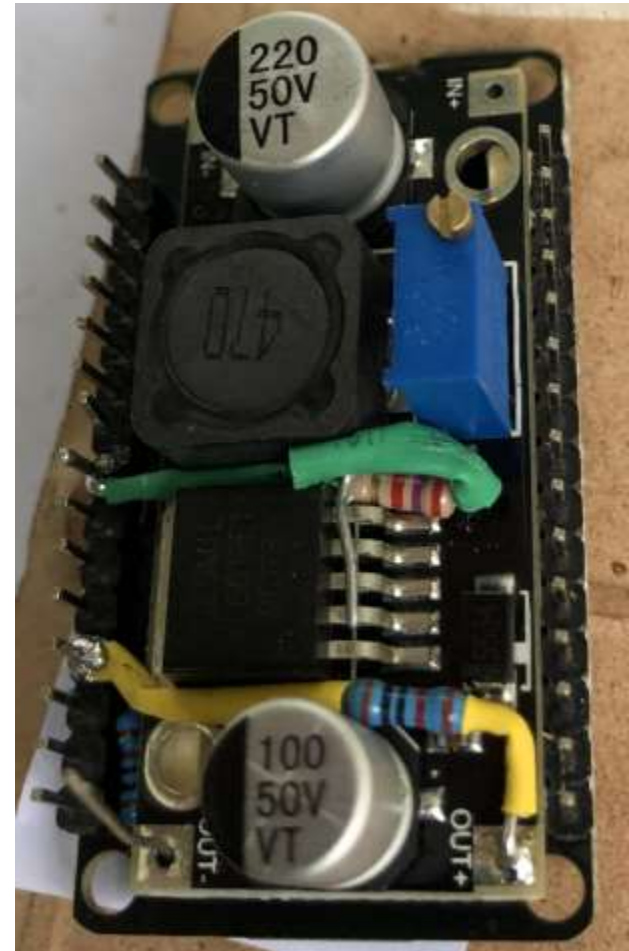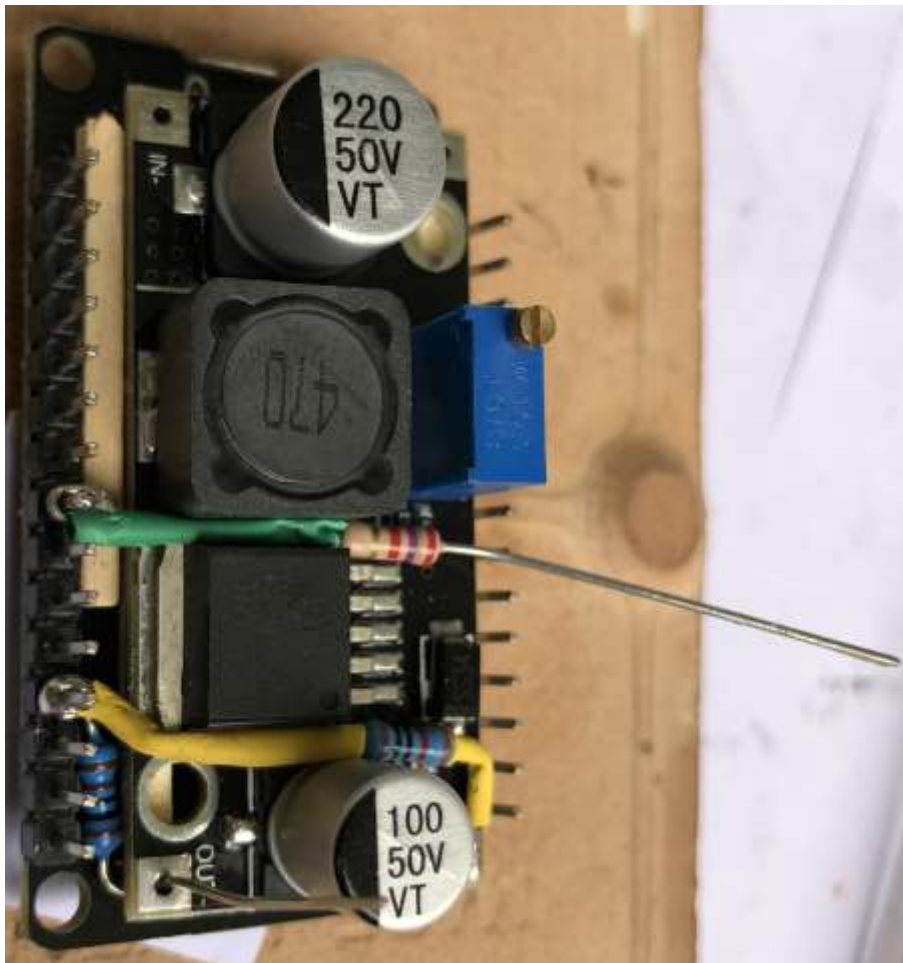
# Mounting 2.7 k $\Omega$ resistor for motor IC error flag EF as input to GPIO pin D25







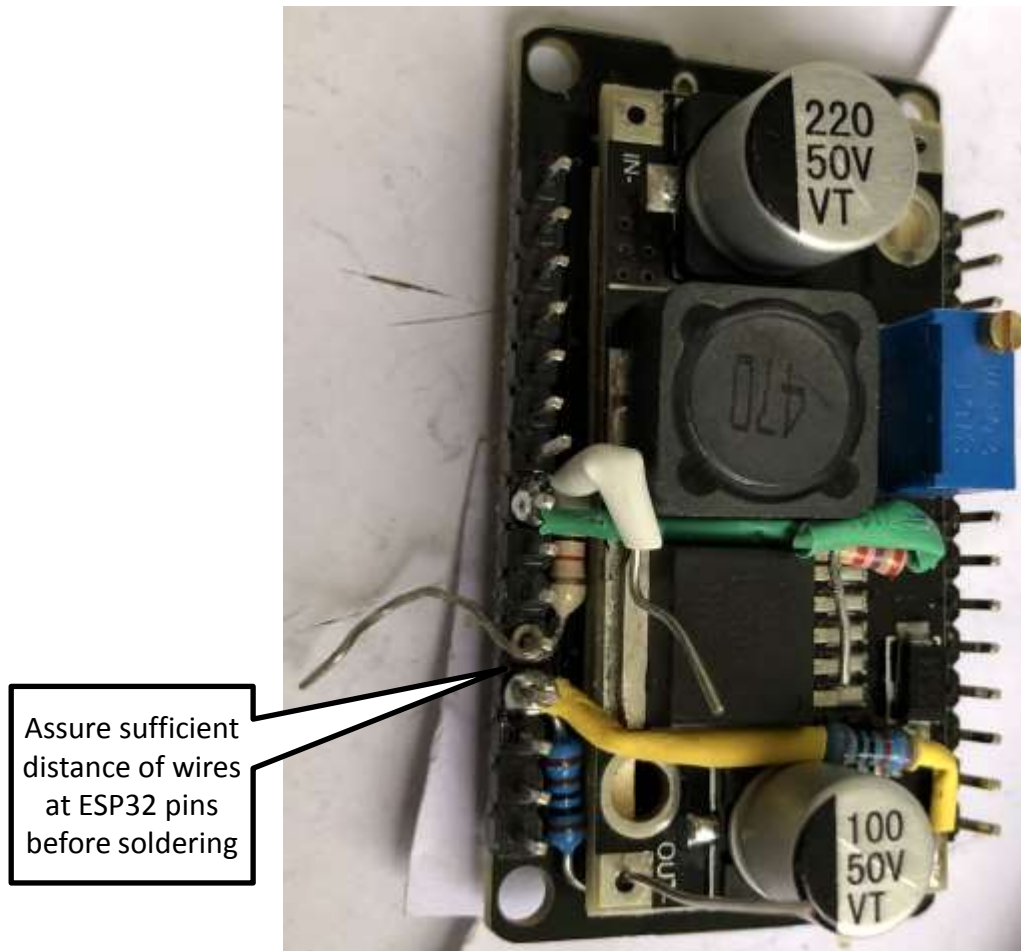
# 1 k $\Omega$ resistor for transfer of motor current measurement to GPIO pin D35





# Motor IC power connection

$V_S$  to +12...16 Vdc at OUT+ and  
GND via 1  $\Omega$  current measuring resistor to OUT-

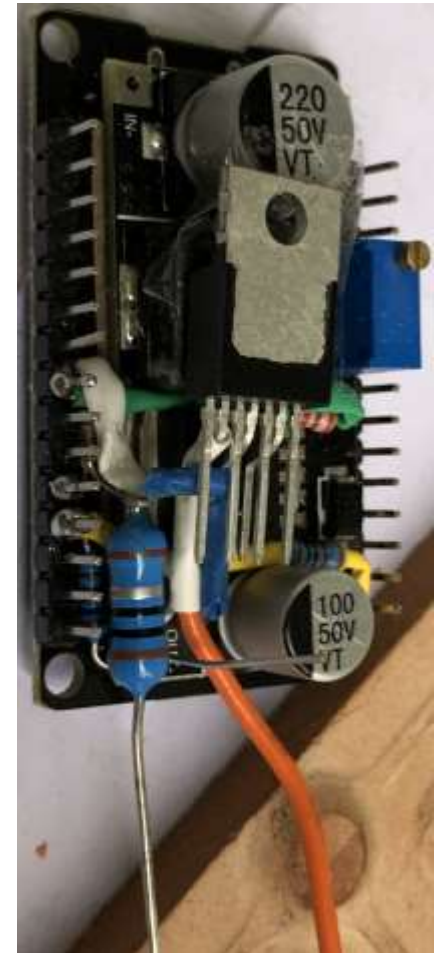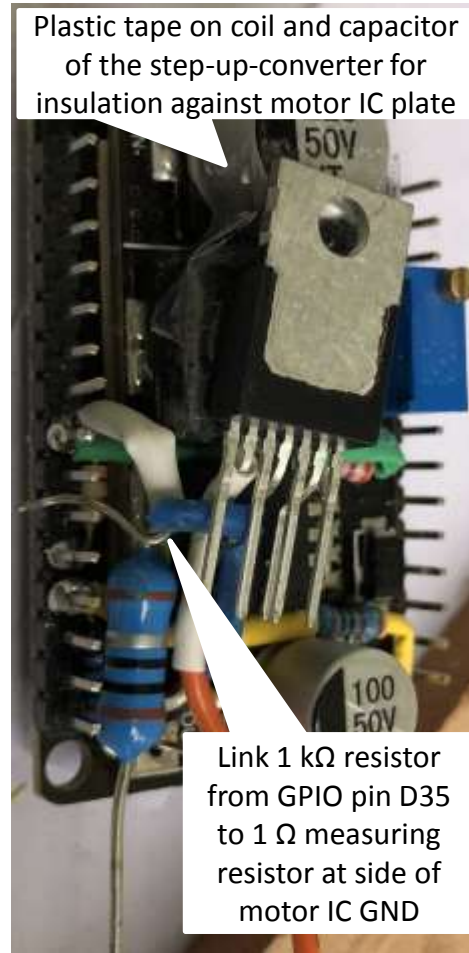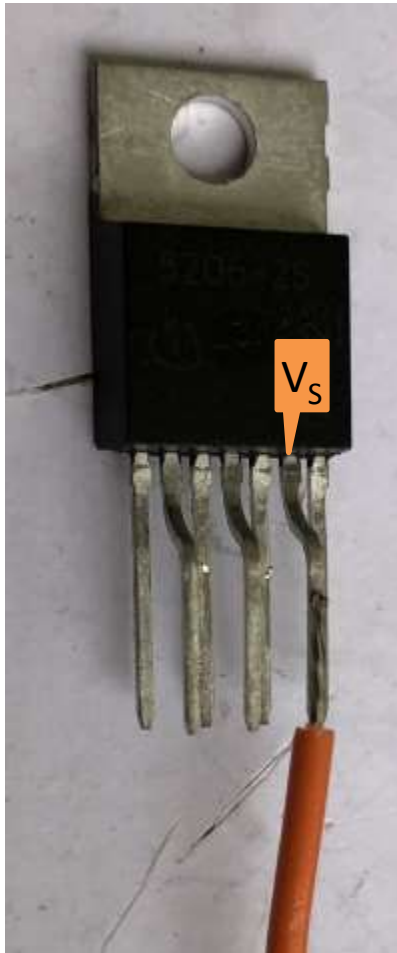


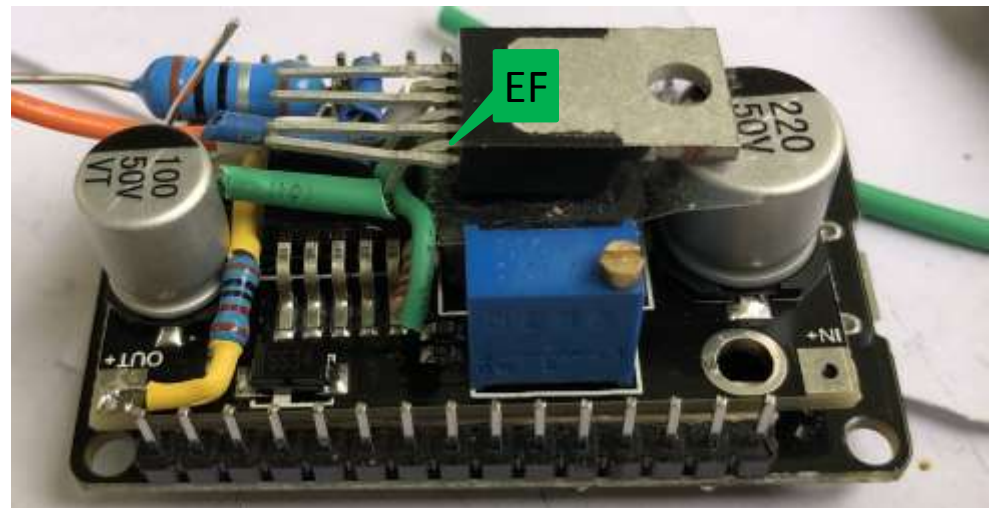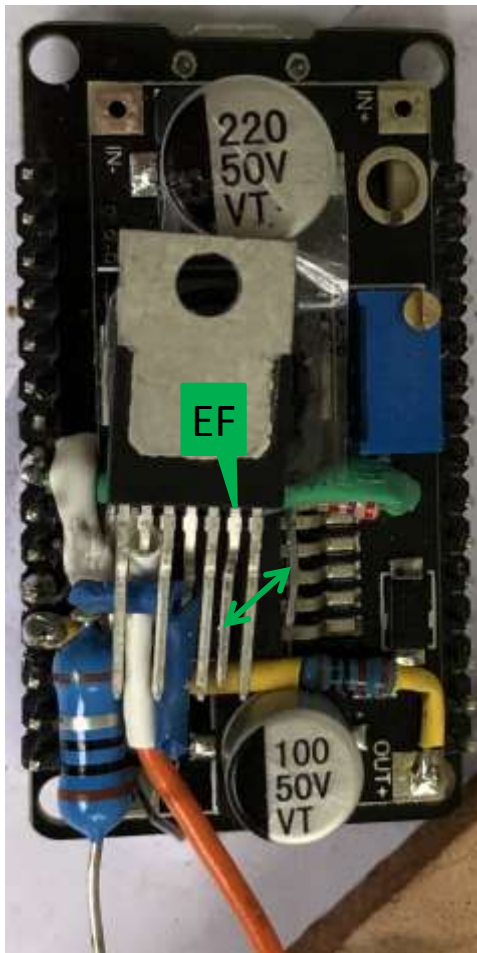Connect 2.7 k resistor to motor IC EF,  
isolate the soldered link with shrink tube






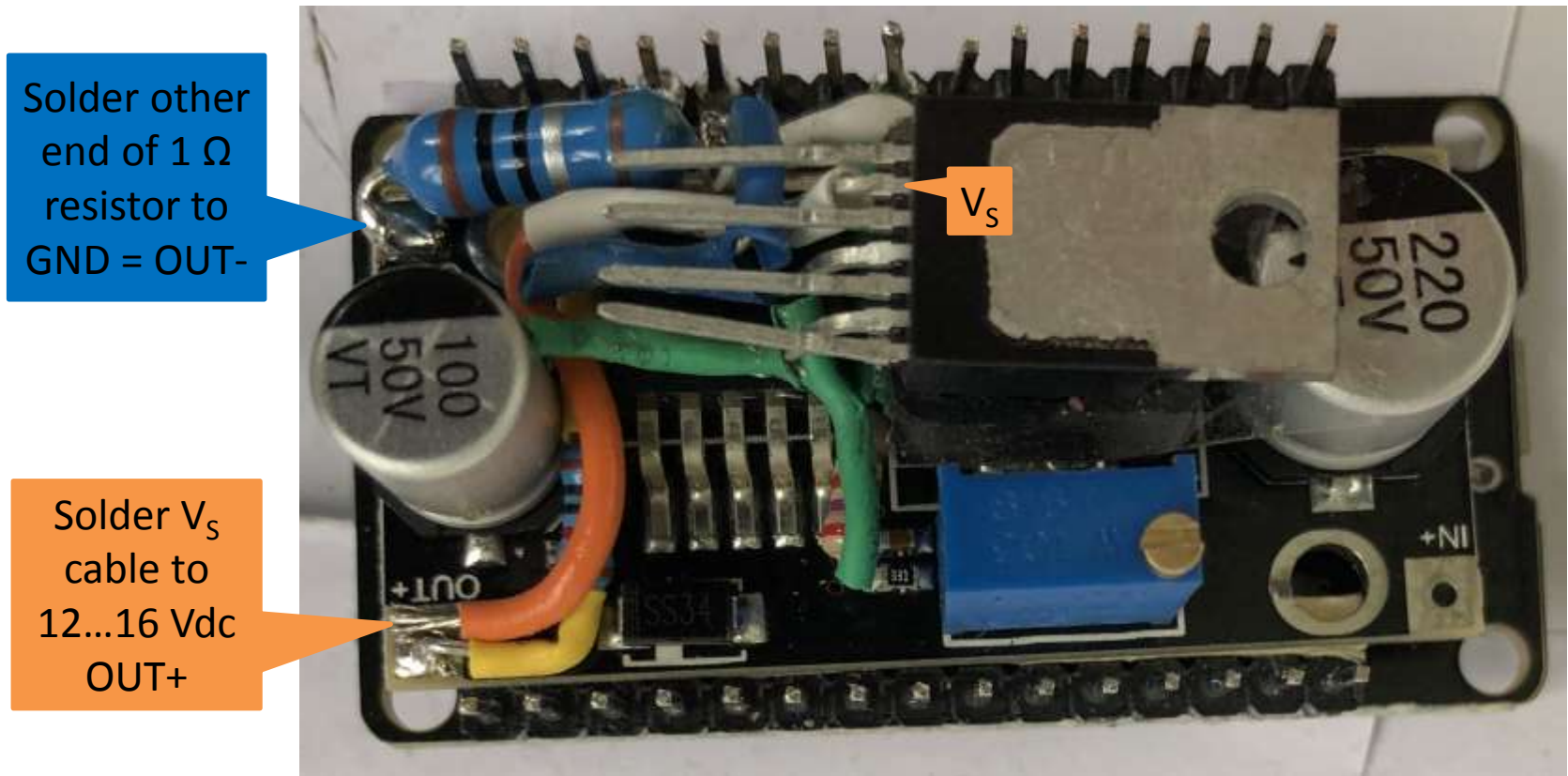
## Connect motor IC to step-up converter output



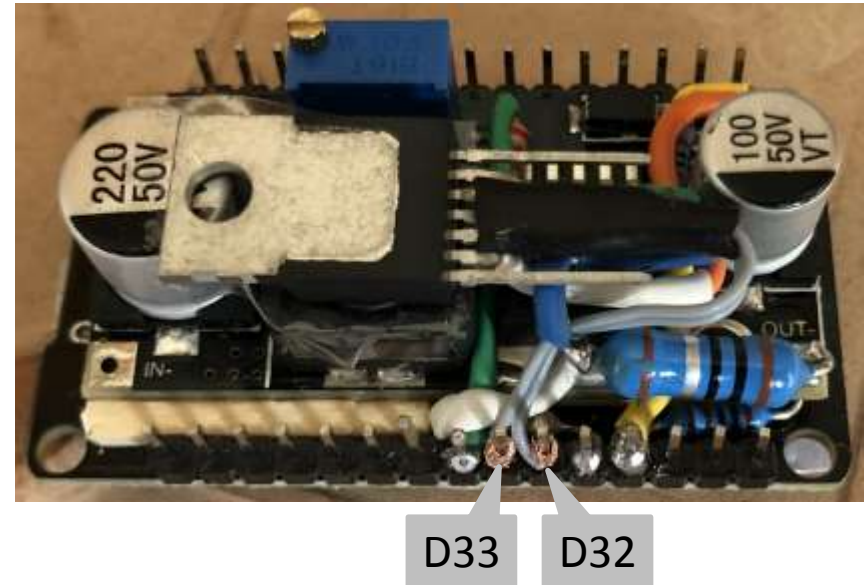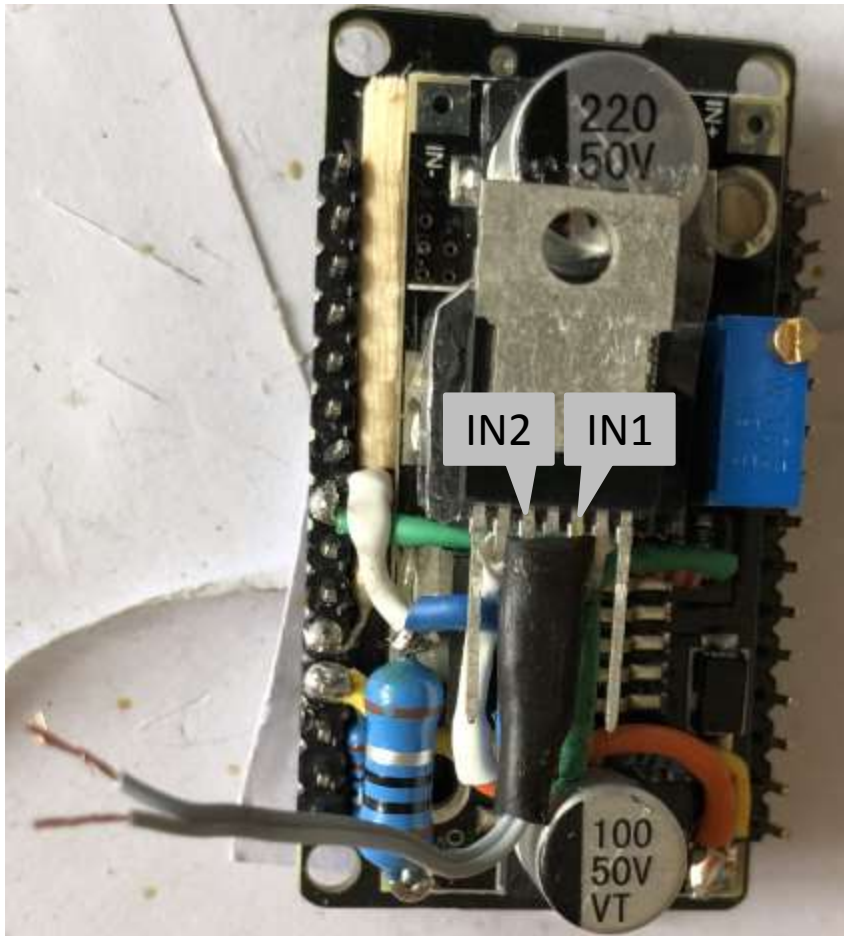
# Connect IN1 and IN2 to GPIO pins D33 and D32



Add appropriate insulation for motor IC input pins with shrink tube

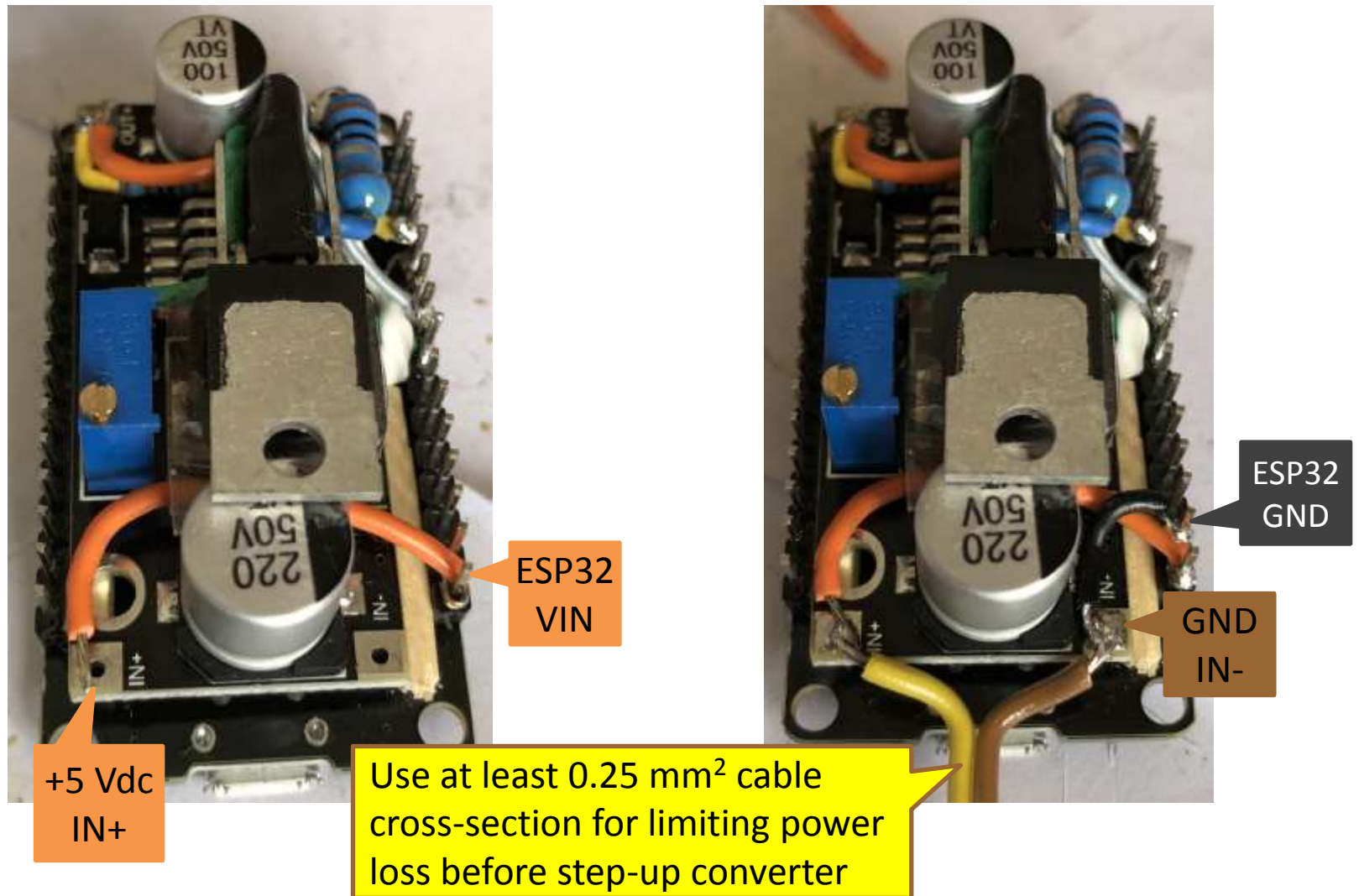Connect 5 Vdc power input of ESP32 and step-up converter to short USB power supply cable.





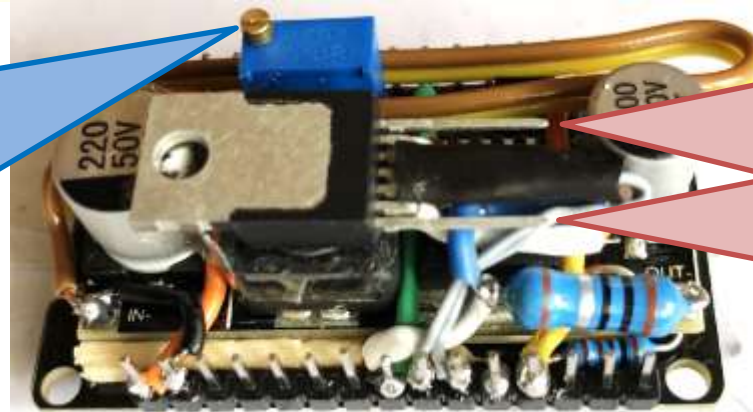
# Install short USB A plug with insulation for connection to USB power bank




The step-up converter output voltage 12 ... 16 Vdc can be adjusted and fine tuned at the potentiometer screw.

Measure the output voltage with multimeter. Correspondingly, set the voltage in the lok.ini file before USB data upload to the ESP32.



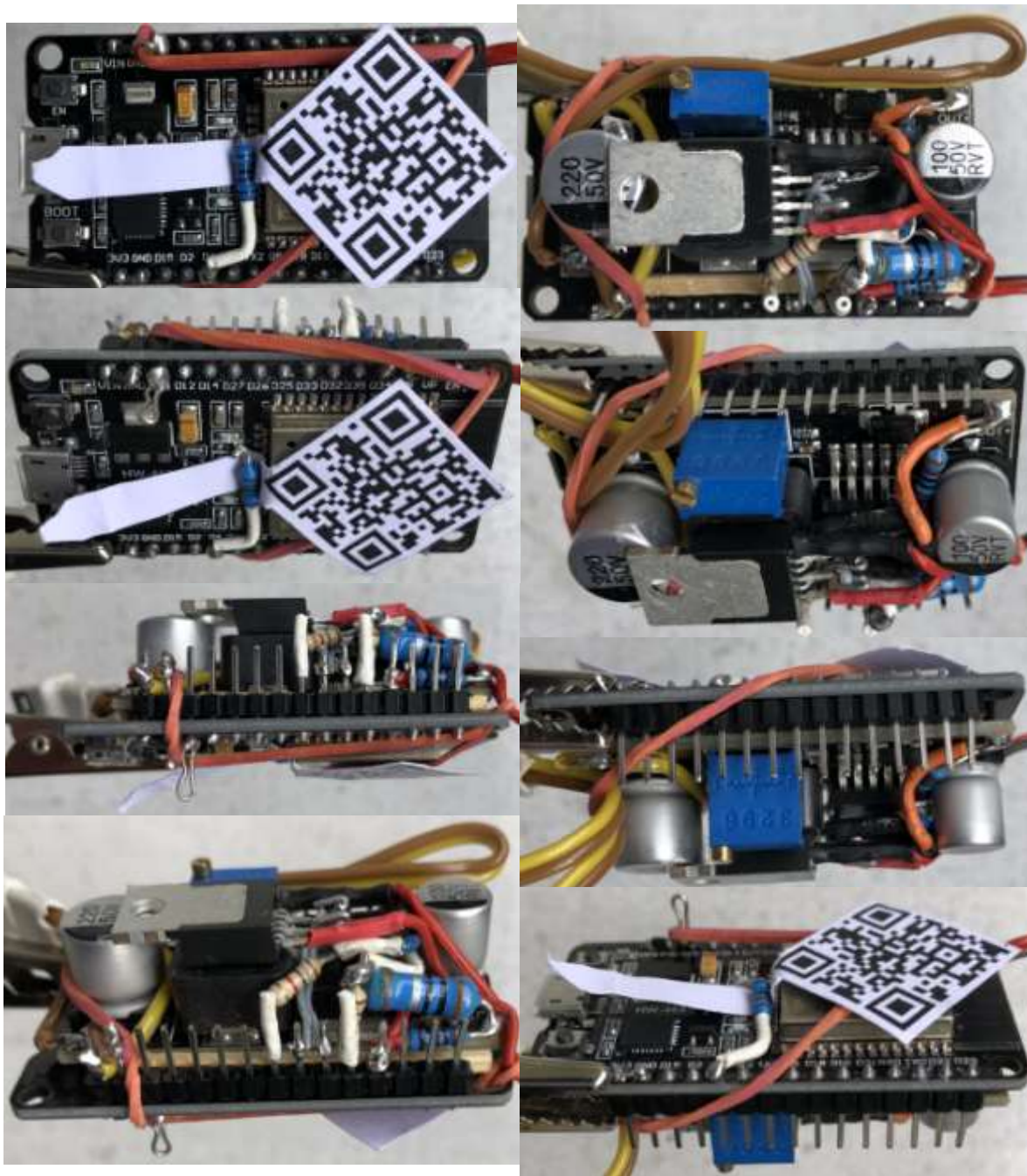Attach thin power cable with mini plug connector from OUT1 and OUT2 of motor IC to locomotive.





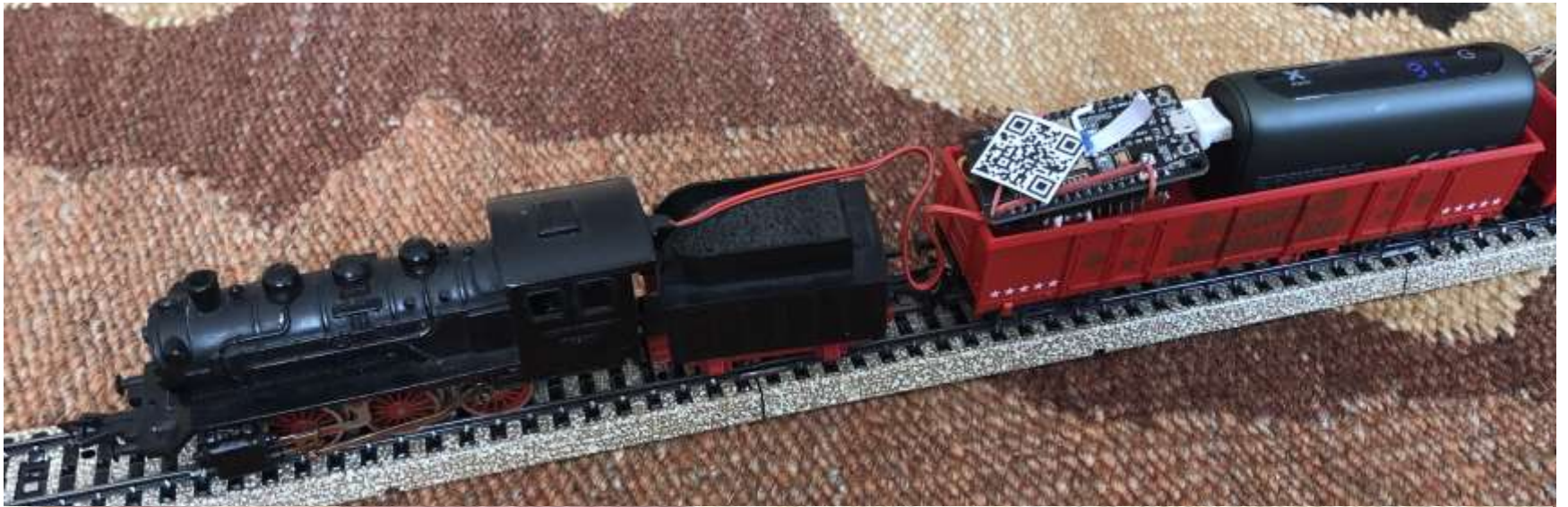
# Fixing cable and electrical connection to locomotive motor







# Option 2: Speedo, speed sampling


by counting railway sleepers with reflective IR sensor



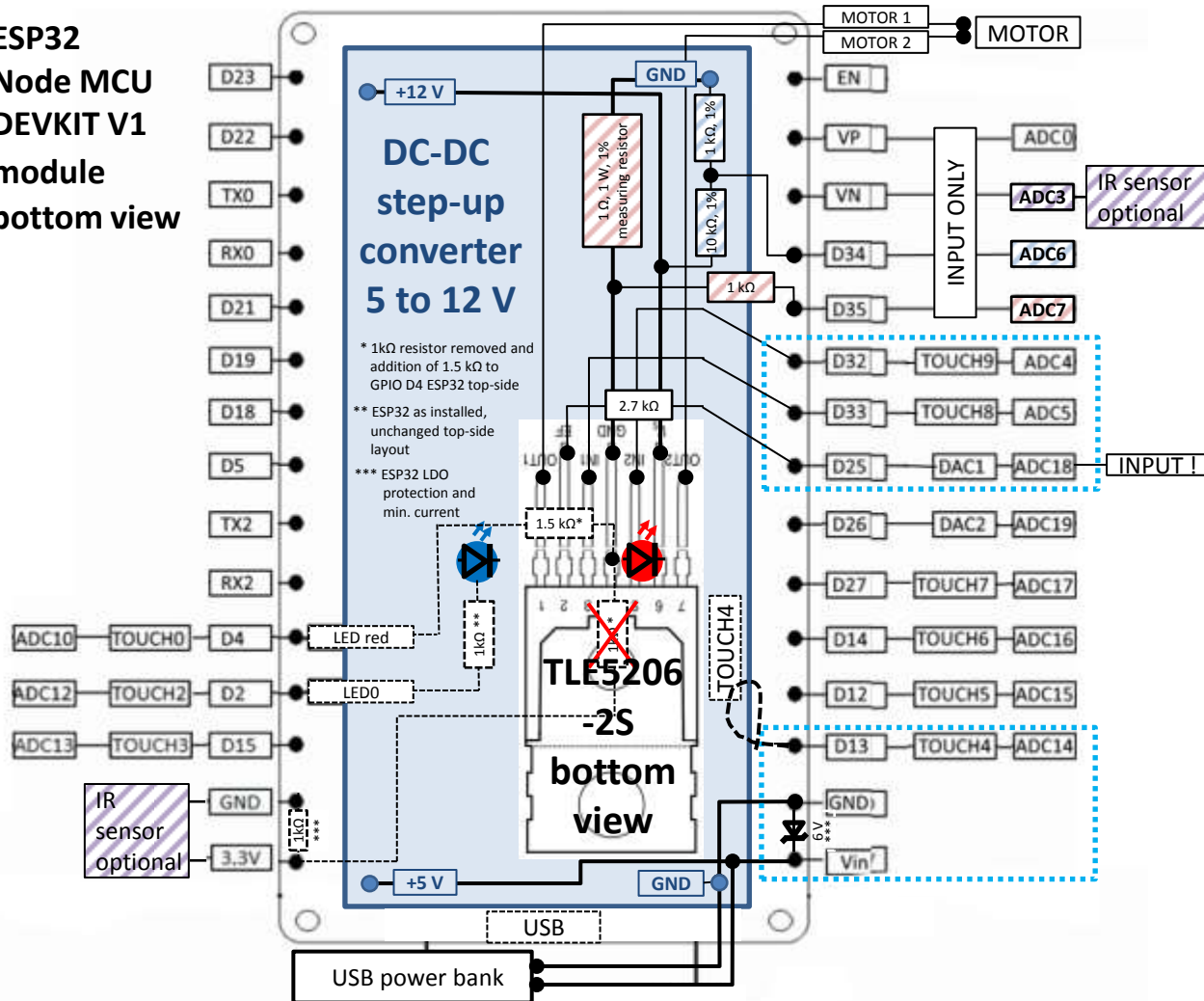
# ESP32 & TLE5206-2S

integrated mounting and wiring with LDO protection, incl. options  
for power data reading & speed measurement by IR sensor


ESP32  
Node MCU  
DEVKIT V1  
module  
bottom view



# Reflective IR sensor

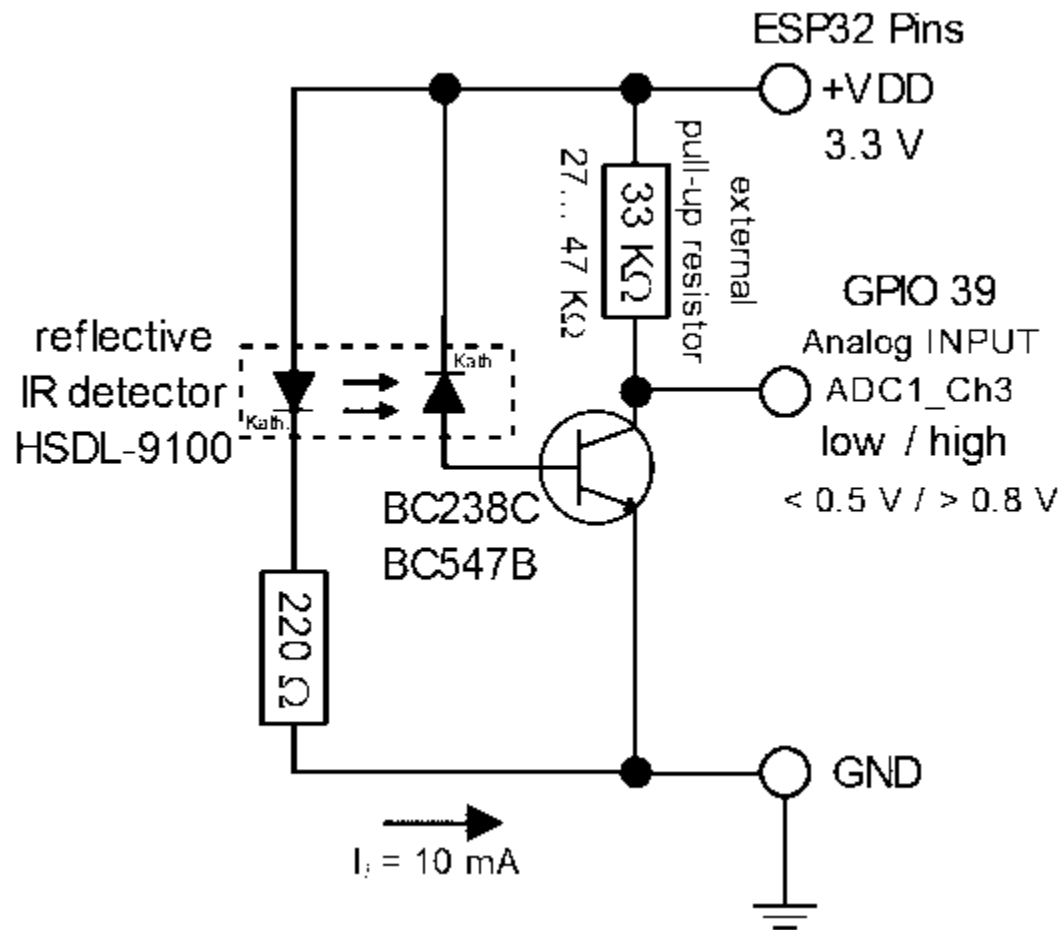
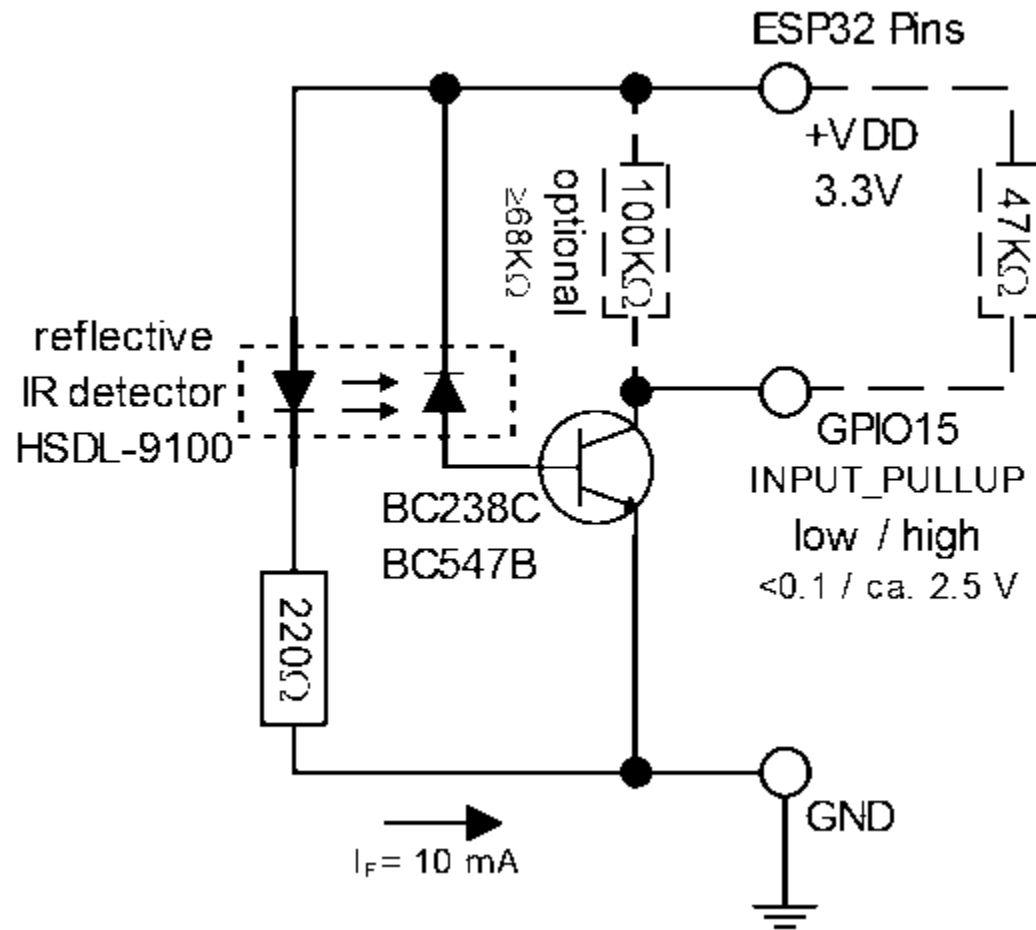
# Reflective IR detector, alternative ESP32 using internal pullup resistor



Alternative implementation with  
motor IC L293D



# ESP32 & L293D

integrated mounting and wiring



# ESP32 & L293D

## integrated mounting and wiring

